

Microprocessors and Microcomputers

All pictures used in the presentation come from
“Microprocessors and Microcomputers” book by Prof. Ing.
Jiří Pinker, CSc.

Ing. Petr Krist, Ph.D.


Department of Applied Electronics and Telecommunications

Faculty of Electrical Engineering, UWB in Pilsen


Contents

- **Basic computer parts and functions**
- **Processor**
- **ALU – instruction overview**
- **Computer circuits**
- **Memory**
- **Interrupts**
- **Timers - counters**
- **Input and output circuits**

Basic Computer Parts

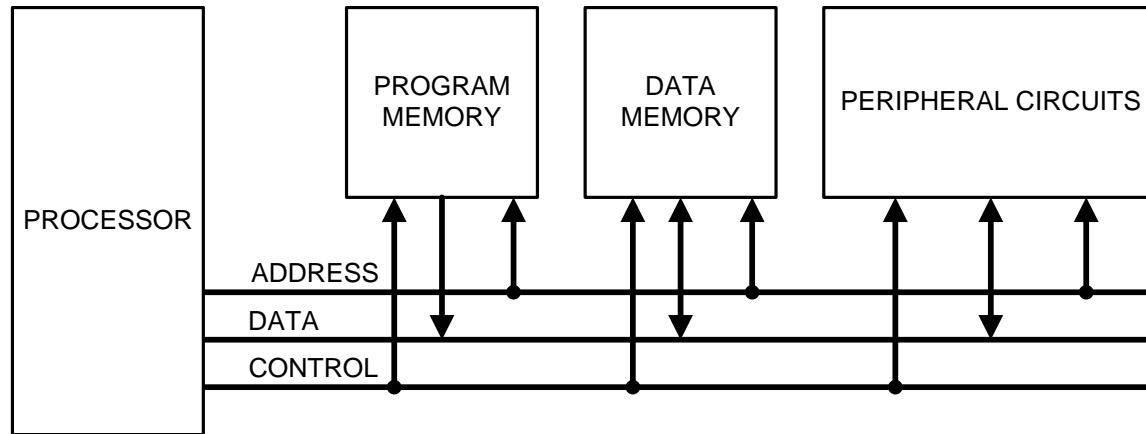


Attachment unit to the bus

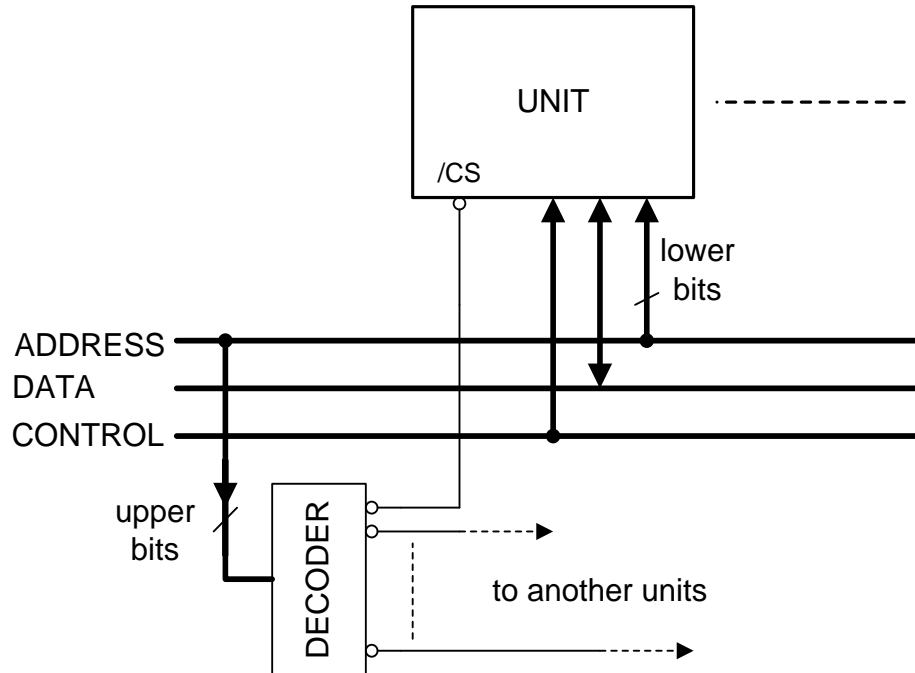

Control signals: **/RD** and **/WR** – usually active in the low level „L“

Peripheral circuit structure

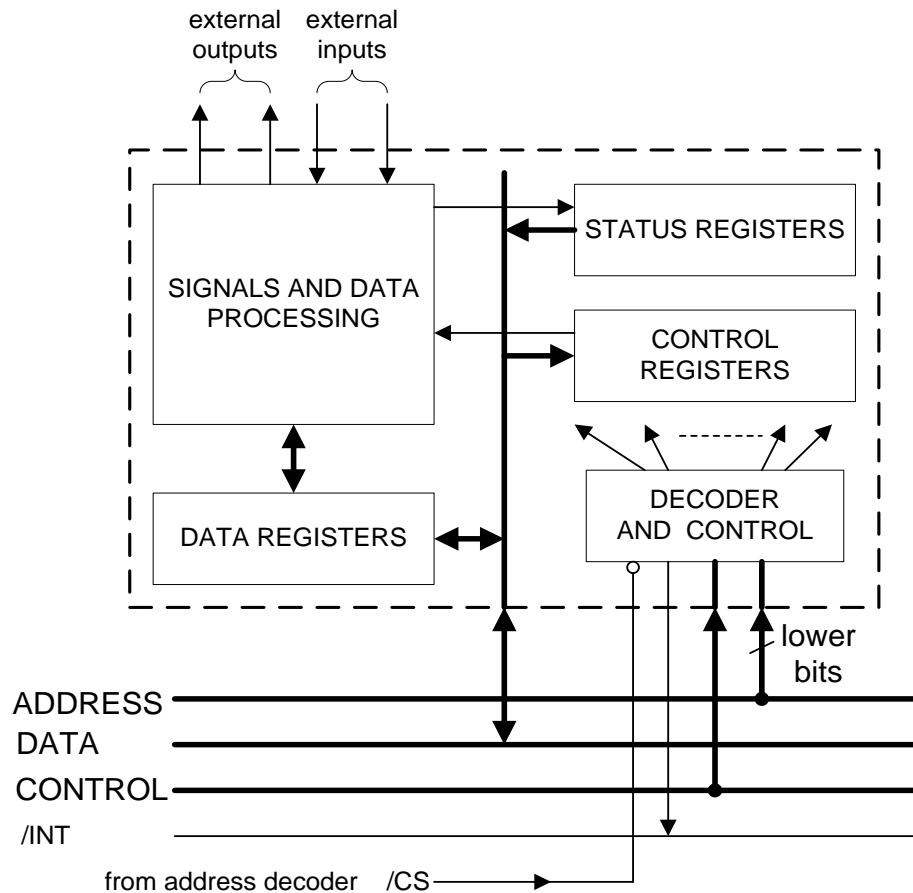


Address space


Set of addresses accessible by one type of the instruction cycle

- **von Neumann architecture** – the only one address space
- **Harvard architecture** – several address spaces: program, data, peripheral I/O


von Neumann architecture

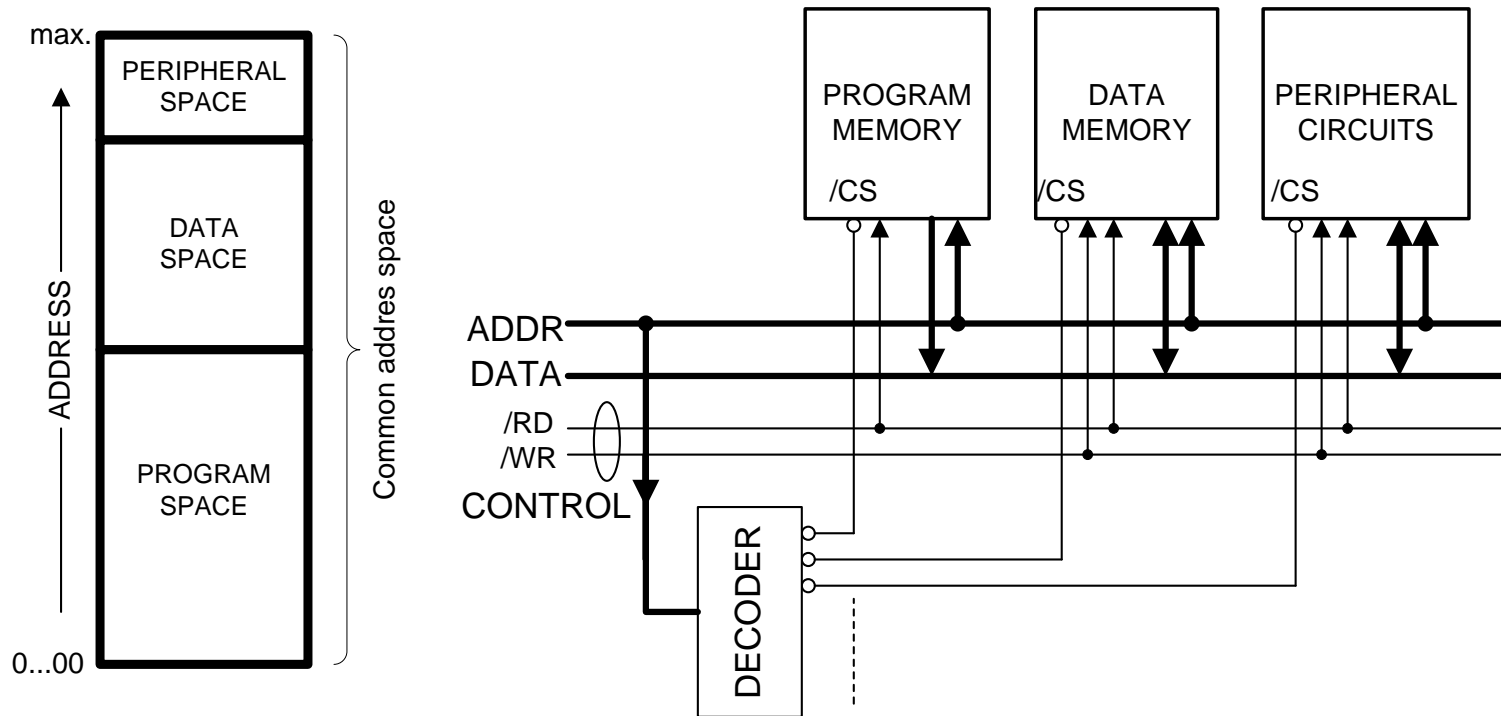

Harvard architecture

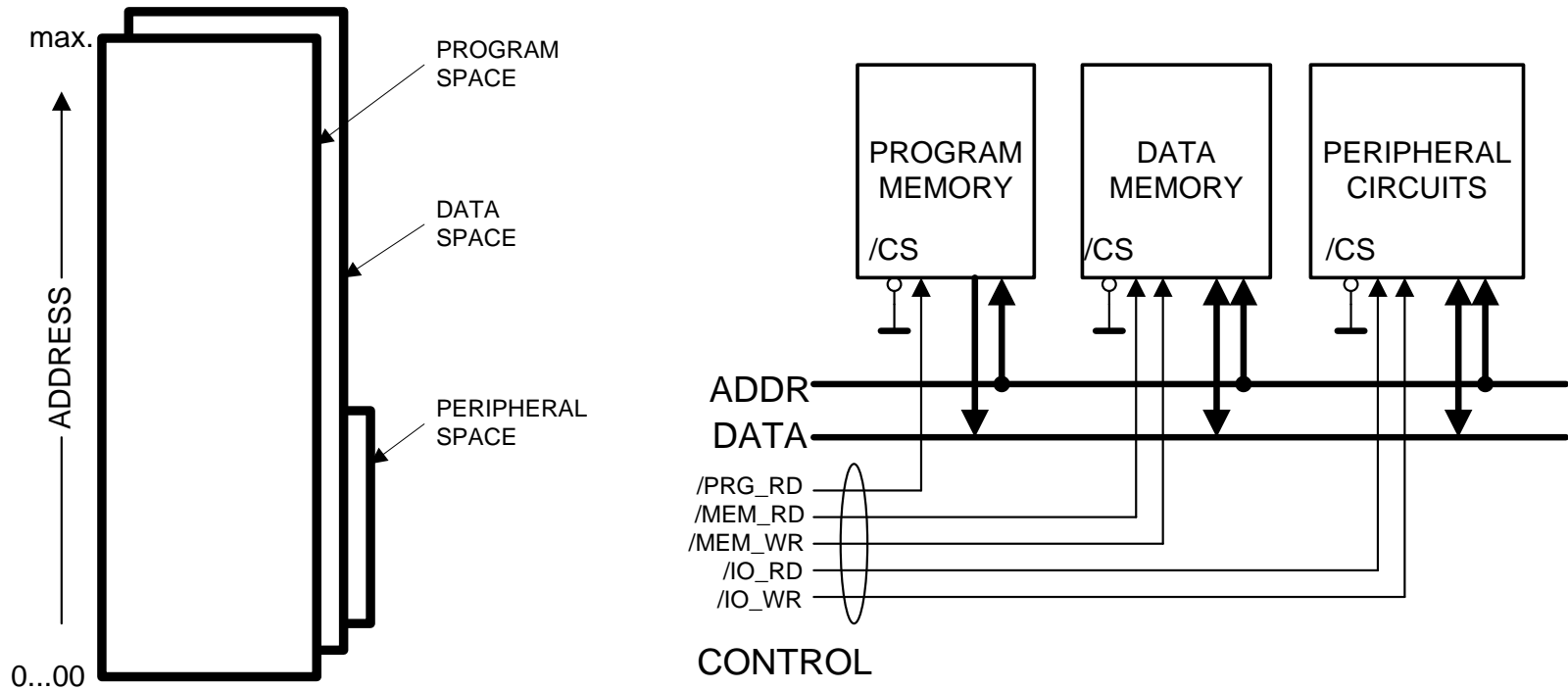

Two-bus system architecture

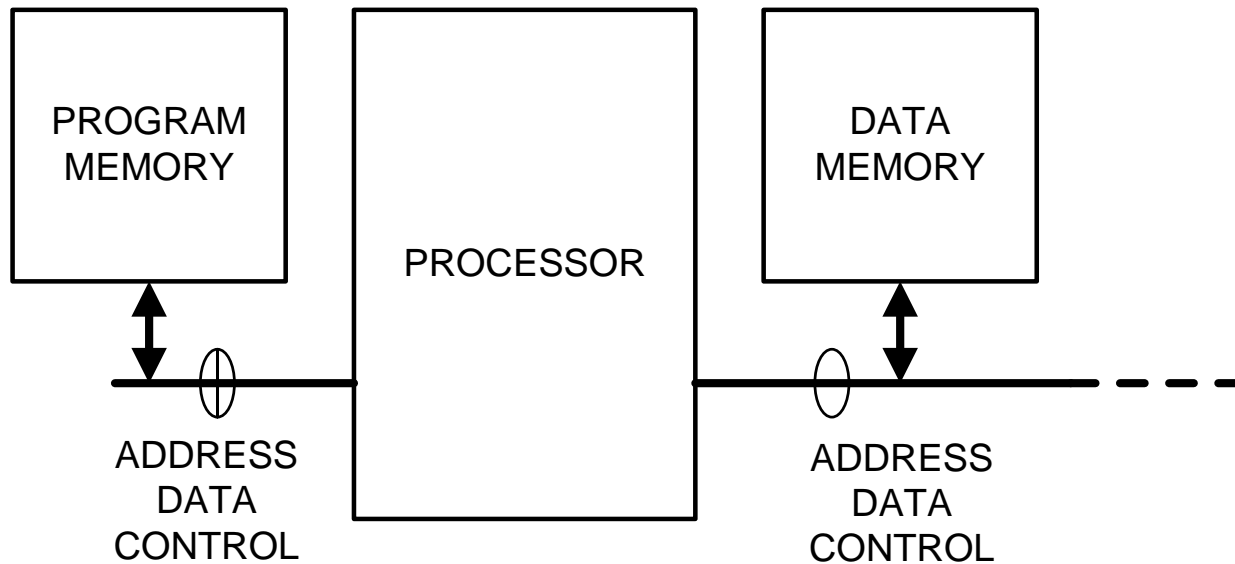

CISC and RISC processors


CISC - Complex Instruction Set Computer

Instruction sets of modern processors are very large. The result of this fact is very complex controller of the processor always implemented in a micro program machine manner.

RISC - Reduced Instruction Set Computer

Processor circuits optimized in order to maximize execution acceleration. The controller is designed like a typical sequence circuit with the emphasize on the maximal speed.

Basic CISC processor circuits

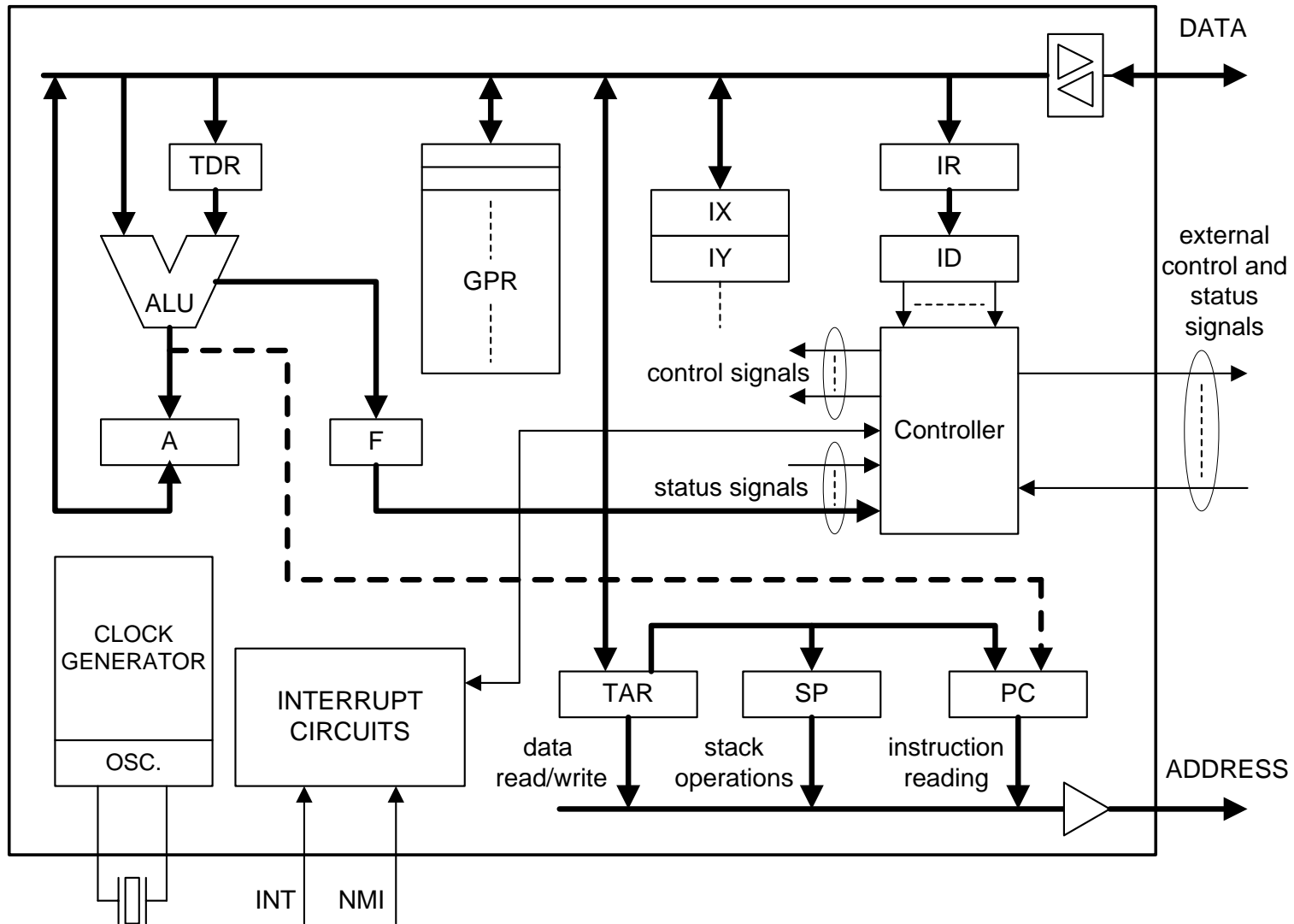

Internal processor structure attributes

PC – Program Counter – holds current program memory address

IR – Instruction register – instruction code storage

TAR - Temporary Address Register – auxiliary address register – address part of instruction storage

TDR - Temporary Data Register – auxiliary data register – data part of instruction storage

IX, IY – Index Registers

ID – Instruction Decoder

GPR – General Purpose Registers – user data registers

F – Flag register – CCR – Condition Code Register

SP – Stack Pointer – LIFO structure

ALU – Arithmetic-logical unit

Arithmetic operations:

addition, subtraction, sign inversion, multiplication and division


Logical operations:

AND, OR, EX-OR, negation, shift and rotation – left, right

Operands – data registers, memory

As a result of an operation is flag bits **F** settings – usually part of **PSW** – Program Status Word

ALU – 1bit implementation example

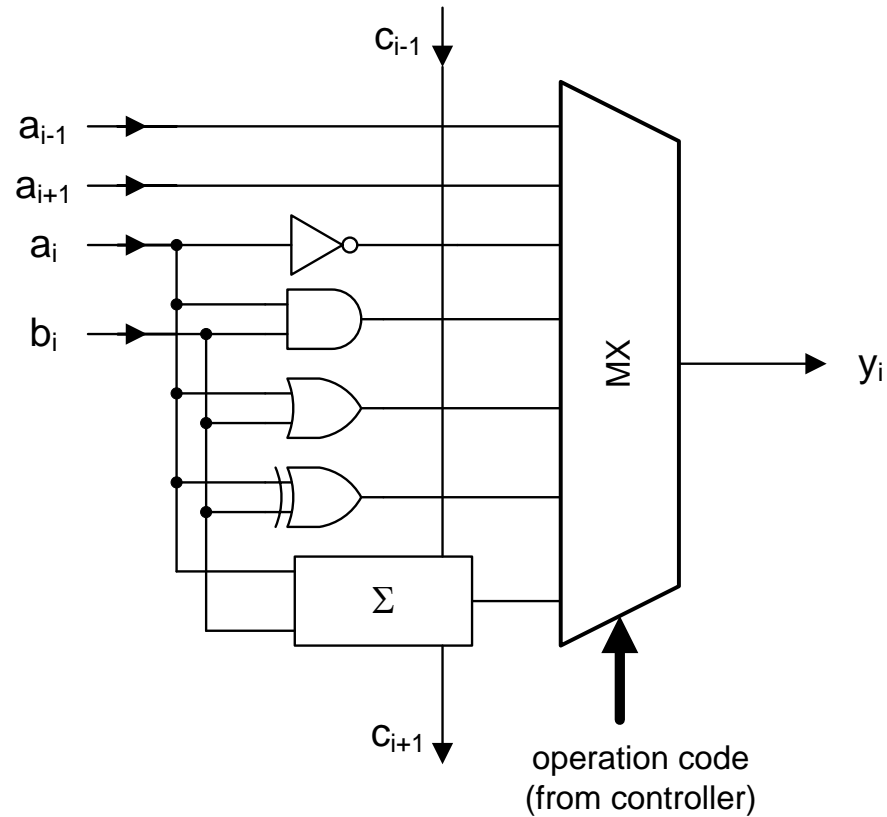

Flag bits

Affected by a result of arithmetic or logical operation, eventually by the content of accumulator – instruction and processor architecture dependent.

Included in the Program Status Word register –**PSW**

C - carry – carry from the MSB bit (unsigned operations)

Z - zero

S - sign (or N – negative)

OV - overflow – result overflow (signed operations)

AC - auxiliary carry – half carry between two nibbles (4 bits)

P - parity


Basic instruction types

- **Data transfer – move instructions**
- **Arithmetic instructions**
- **Logical instructions**
- **Bit operations instructions**
- **Shift and rotation instructions**
- **Stack operations instructions**
- **Jump instructions**
- **Functions calling and return instructions**
- **Input and Output instructions**
- **Processor control instructions**


Basic instruction parts



INC R0

 


ST R0, address

 


LD R1,#data

Instruction execution

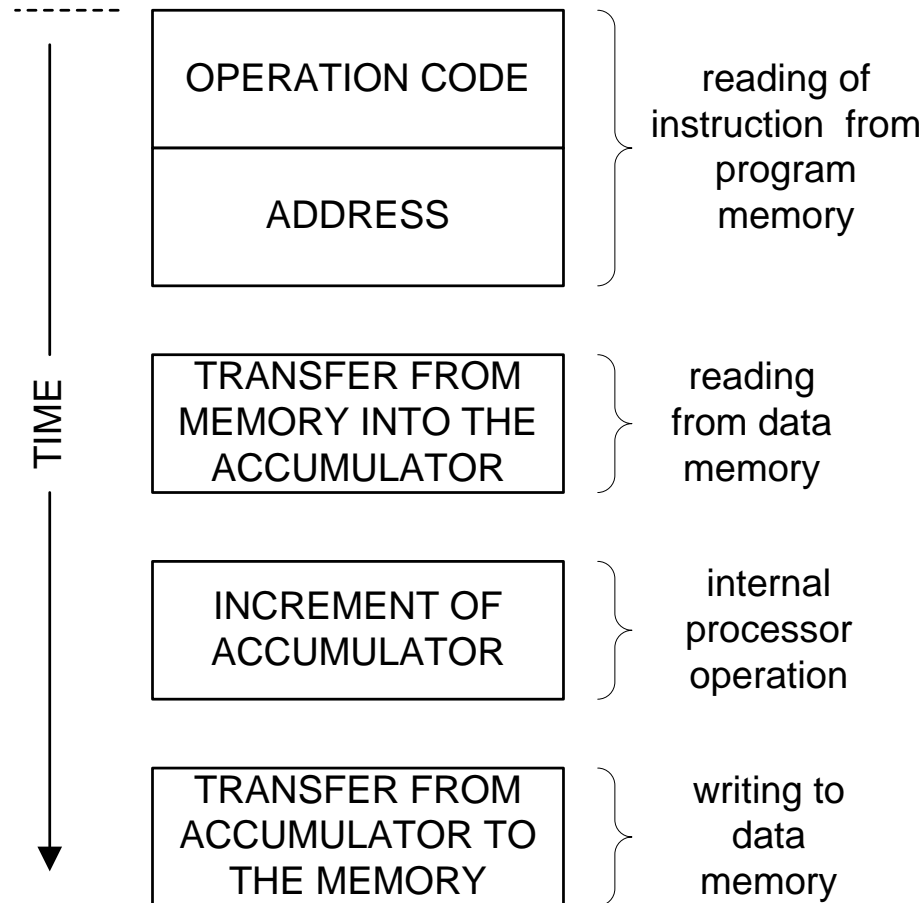„increment contents of the memory at the address..“




Stack pointer - SP

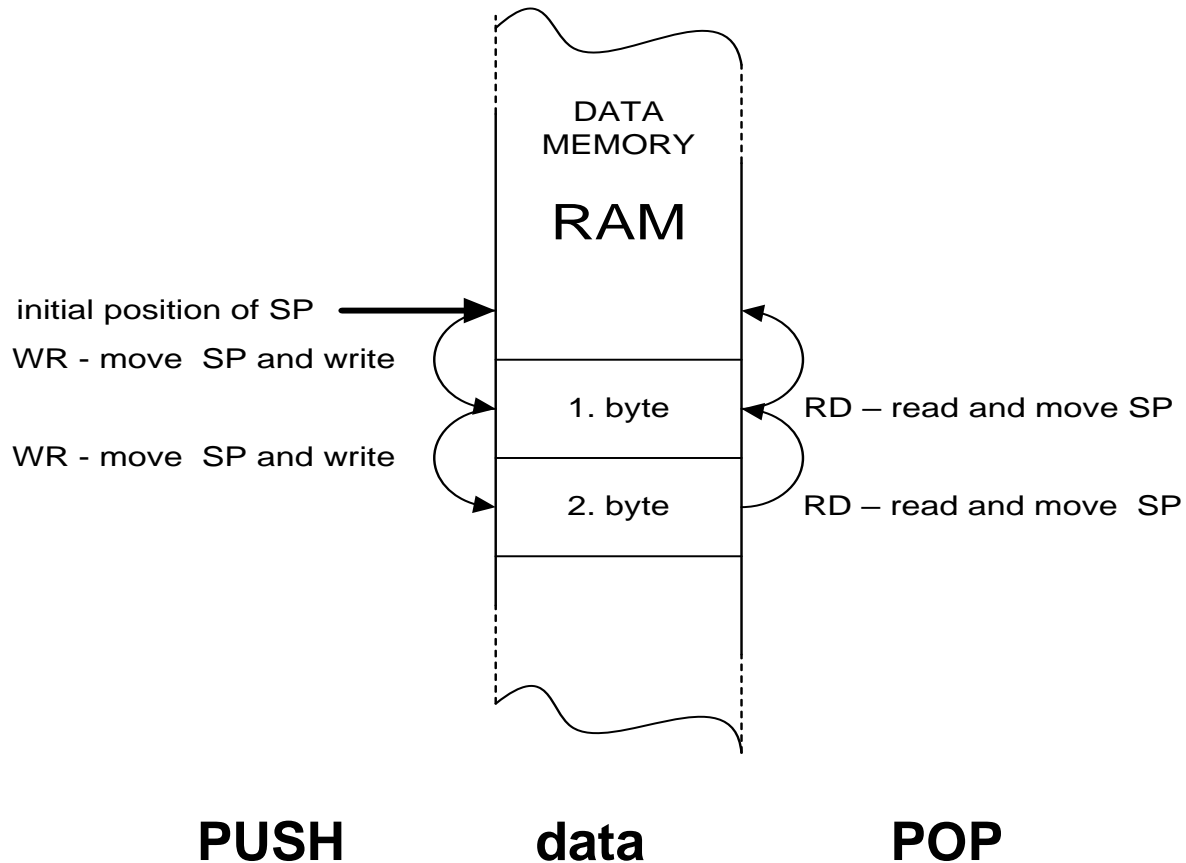

Saving of subroutine and ISR (Interrupt Service Routine) return addresses

Stack Pointer - SP

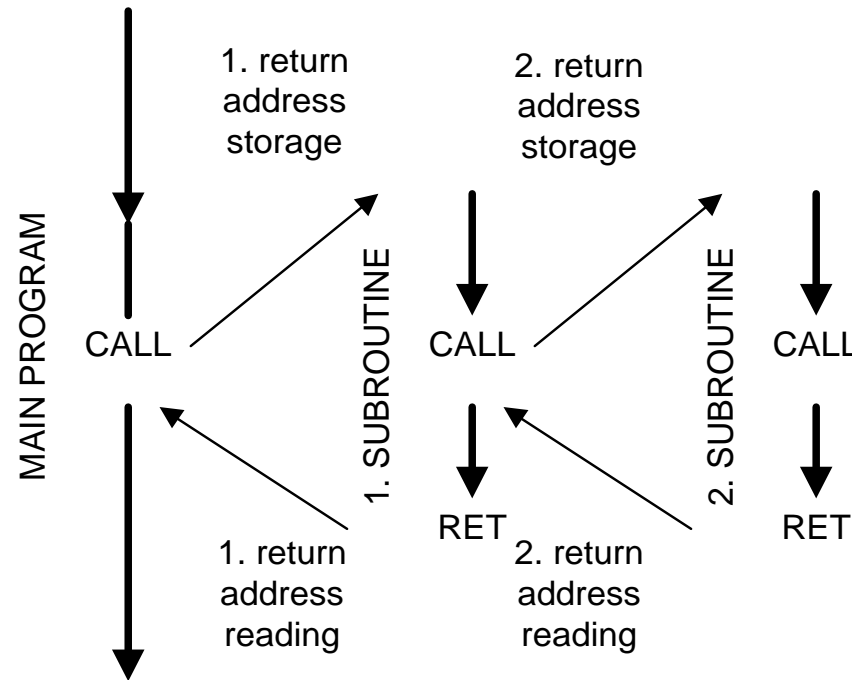

- **SP must** be initialized prior the first usage !!!
- **Look-out** stack overflow - underflow !!!

Processor execution acceleration

OP code reading from ROM	decoding	reading of address operand from ROM	RAM address generation	operand reading from RAM	arithmetic/logic operation execution	next instruct.
--------------------------	----------	-------------------------------------	------------------------	--------------------------	--------------------------------------	----------------

Simple processor – execution sequence

← instruction cycle				
→				
reading + decoding of instruction 1	instruction 1 execution	reading + decoding of instruction 3	instruction 3 execution	
	reading + decoding of instruction 2	instruction 2 execution	reading + decoding of instruction 4	instruction 4 execution

Two-phase instruction overlapping - pipeline

Computer circuits

Multichip computer

All necessary function units are external with regard to processor

- design complexity, larger space
- HW configuration flexibility

Single-chip microcomputer

All components integrated on the chip. Predefined internal structure

- compactness, space savings.
- configuration and initialization by using large amount of control registers
- number of I/O pins of the device limited – shared I/O and peripheral functions

Computer circuits interconnection

Bus system is used to interconnect processor to the other computer circuits – address, data and control bus


External bus signals and their timing knowledge is necessary to design system of external circuits.

Data exchange provided by **bus cycles**:


- memory read cycle
- memory write cycle

Control bus signals generated by system controller

External system controller

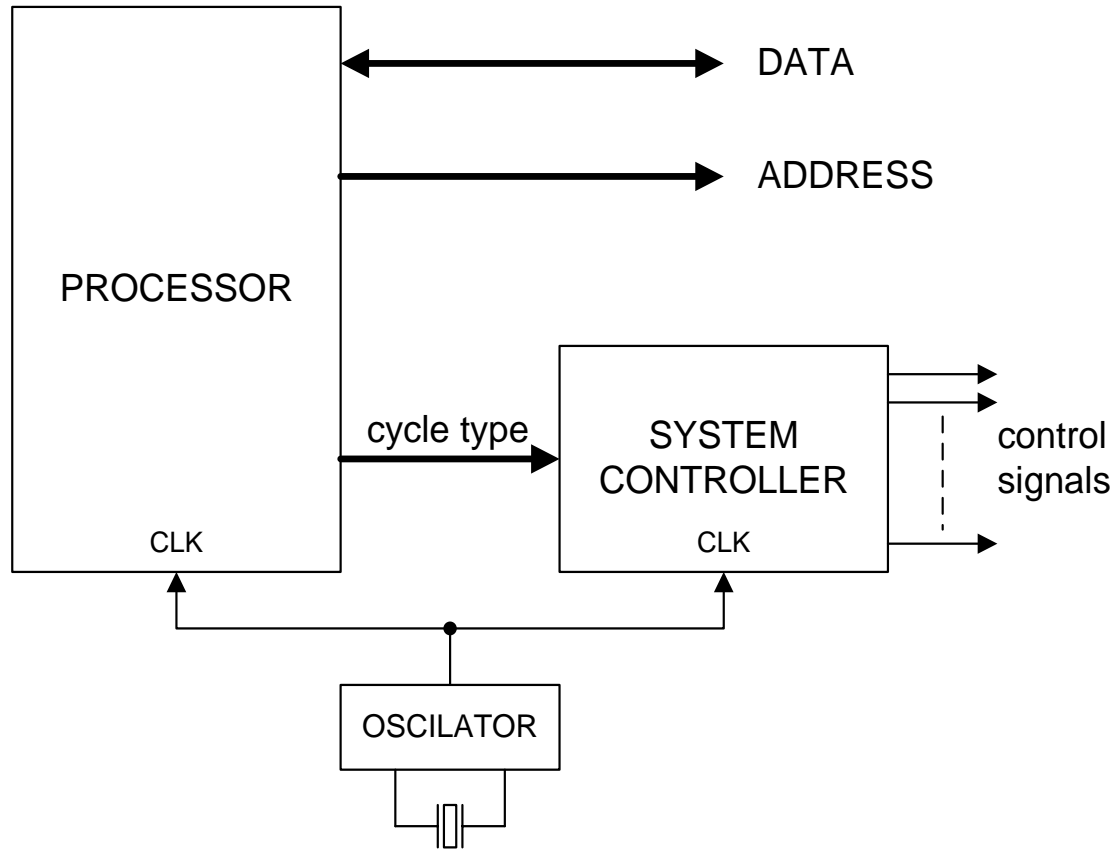

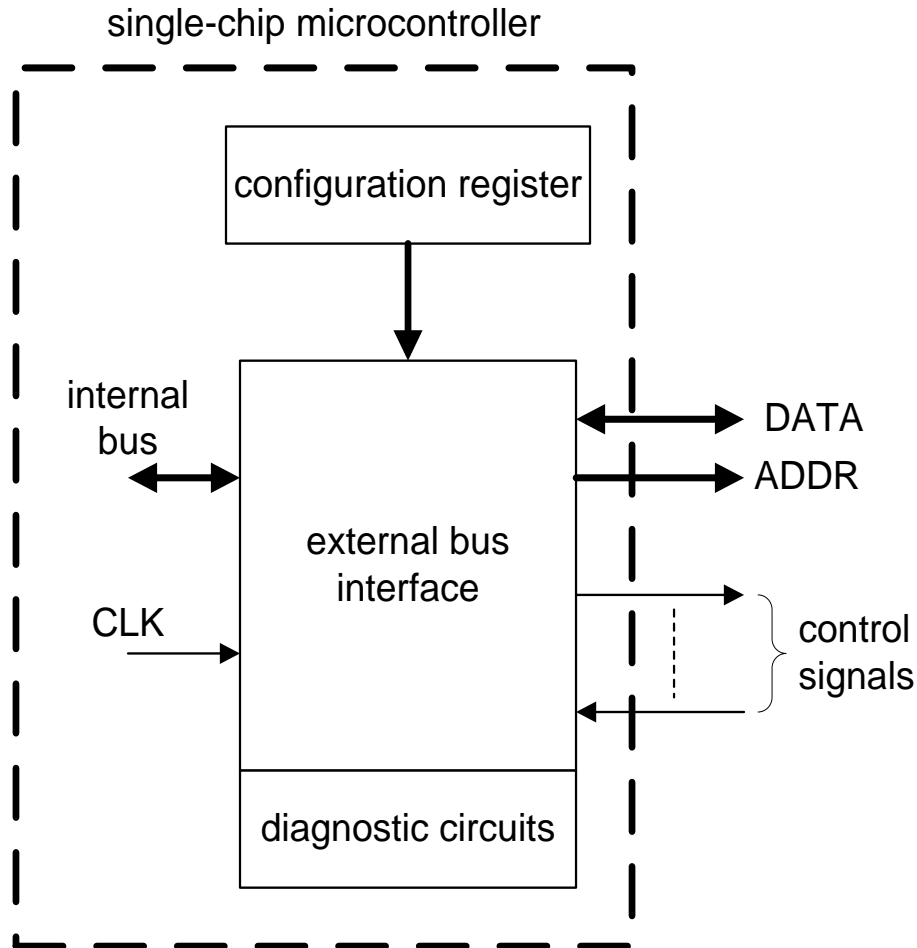Internal system controller of the single-chip microcontroller



Any possible external circuit extension is solved using address, data and control bus pins.

To avoid excessive number of device pins these external buses often share pins with other peripheral functions or general purposed parallel inputs/outputs - GPIOs


Configuration register - single-chip microcontroller

Operation mode - 16-bit or 8-bit width data bus, address and data bus multiplex, timings, signals polarity, wait states...


External bus operation mode is possible to be changed through the system controller programming - equipped with **configuration register** for these purposes.

Configuration register – initiated and affected by the sampled status of particular pins during reset on power up (/EA), eventually consecutively by the initiation program routine.

 
Example – configuration settings using I/O pins




Unit connection to external buses

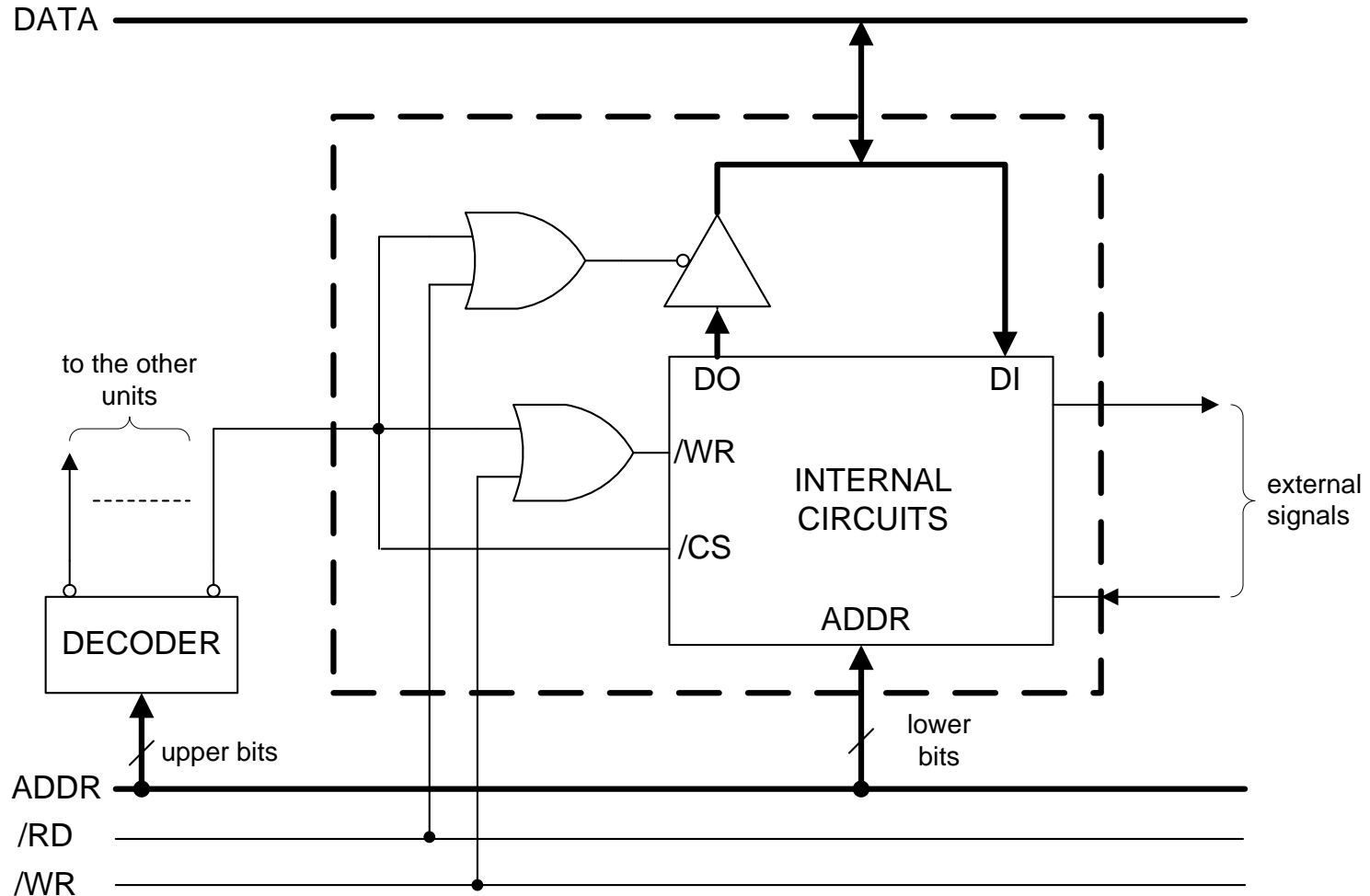

Basic bus cycles

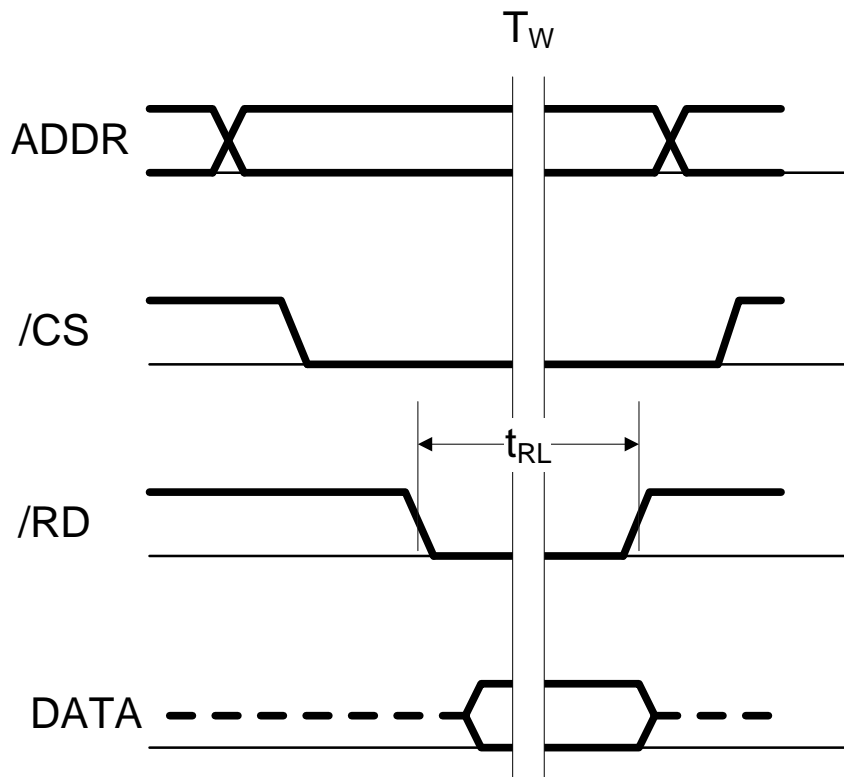


Read cycle

 



Write cycle

Wait states - READY- WAIT

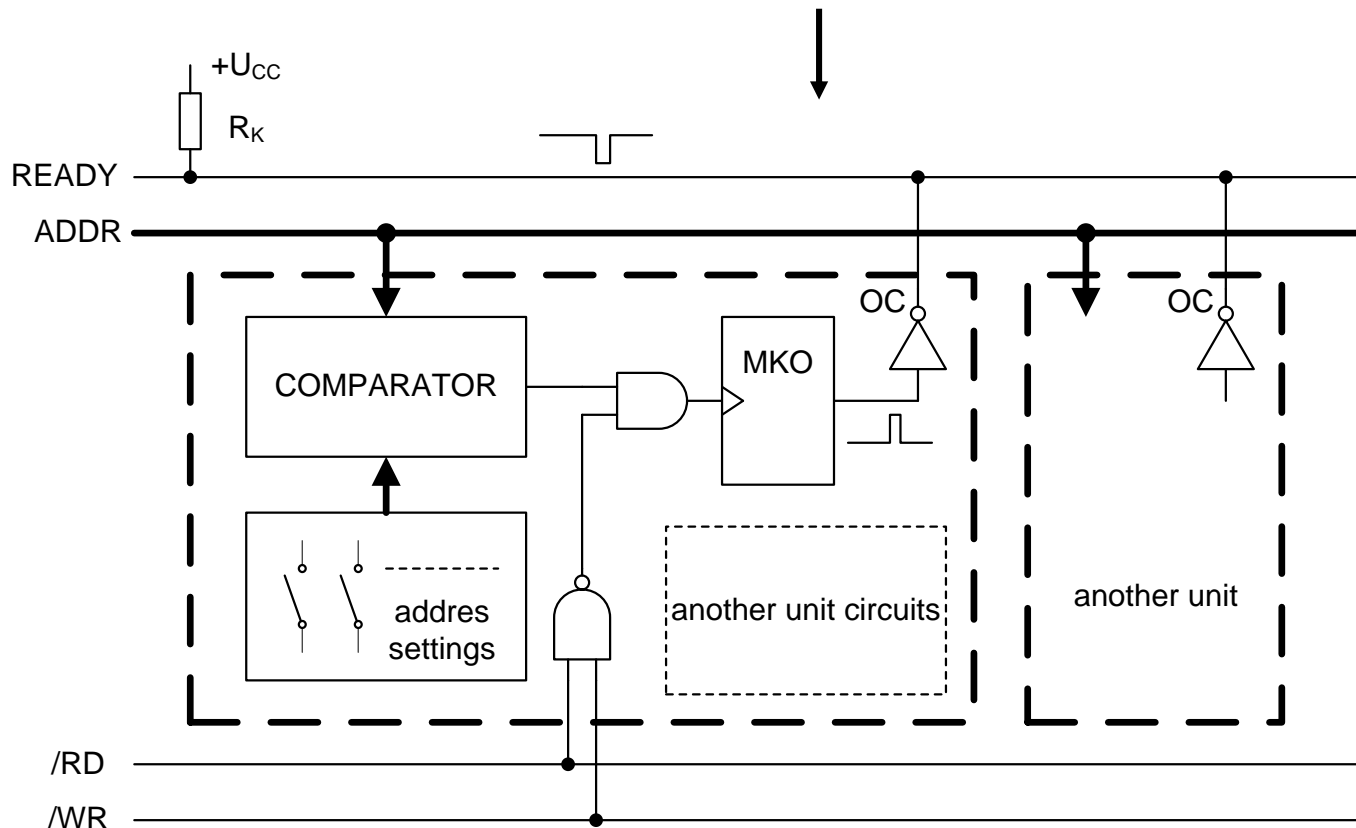- Central control – Wait-State Generator
- Decentralized timing circuits





Multiplexed bus

 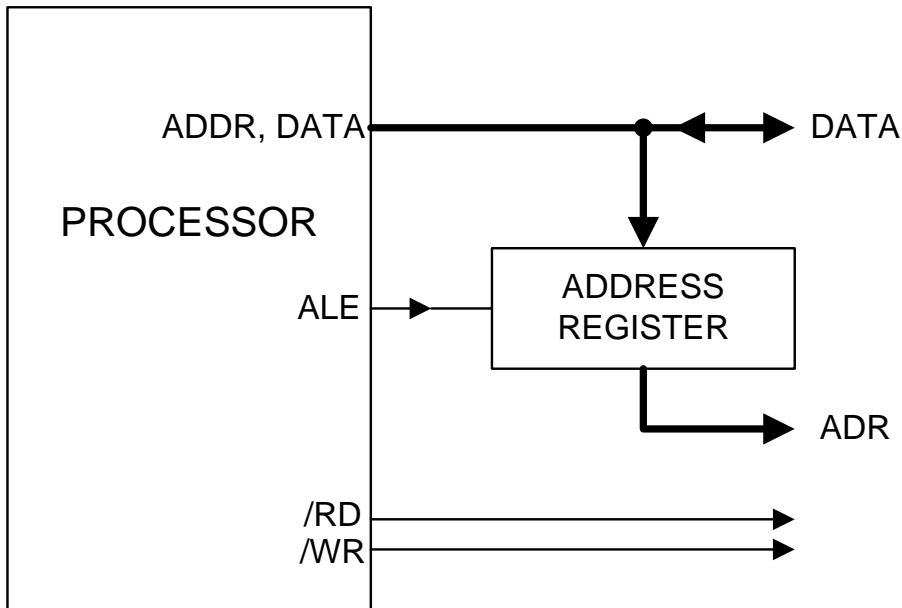

- To save number of device pins
- Bus cycle slows down as a result of address latching



External memory connection - byte, word

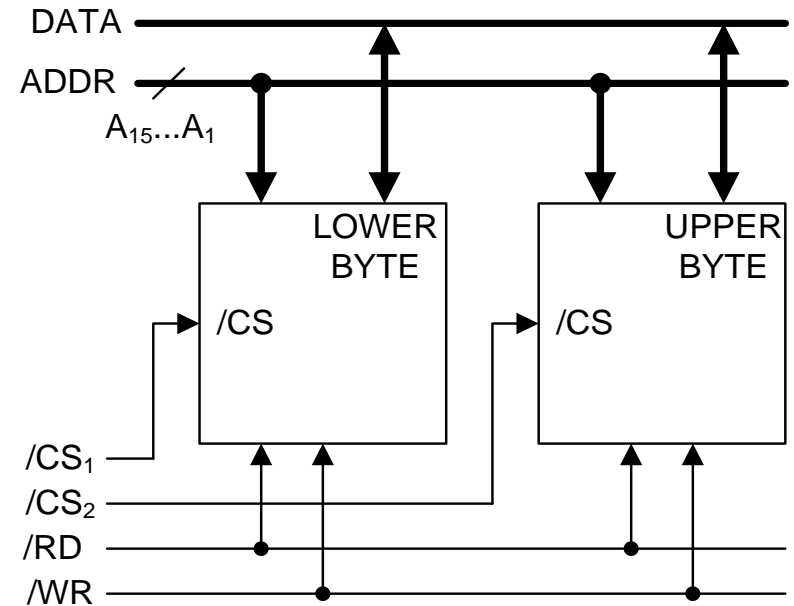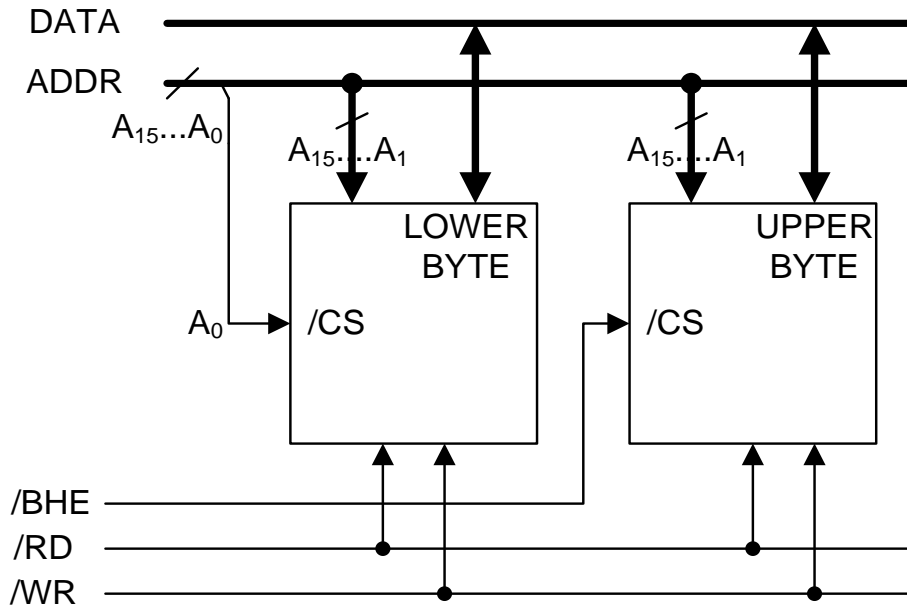


- In the case of **16-bit data bus** the external units can operate either full data width or 8-bit data width
- Possible transfer of **upper byte**, **lower byte**, or both of them at the same time – **complete word**

Address decoder and select logic


ADDRESSA

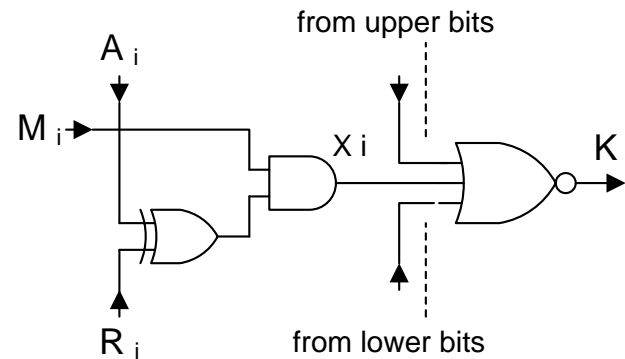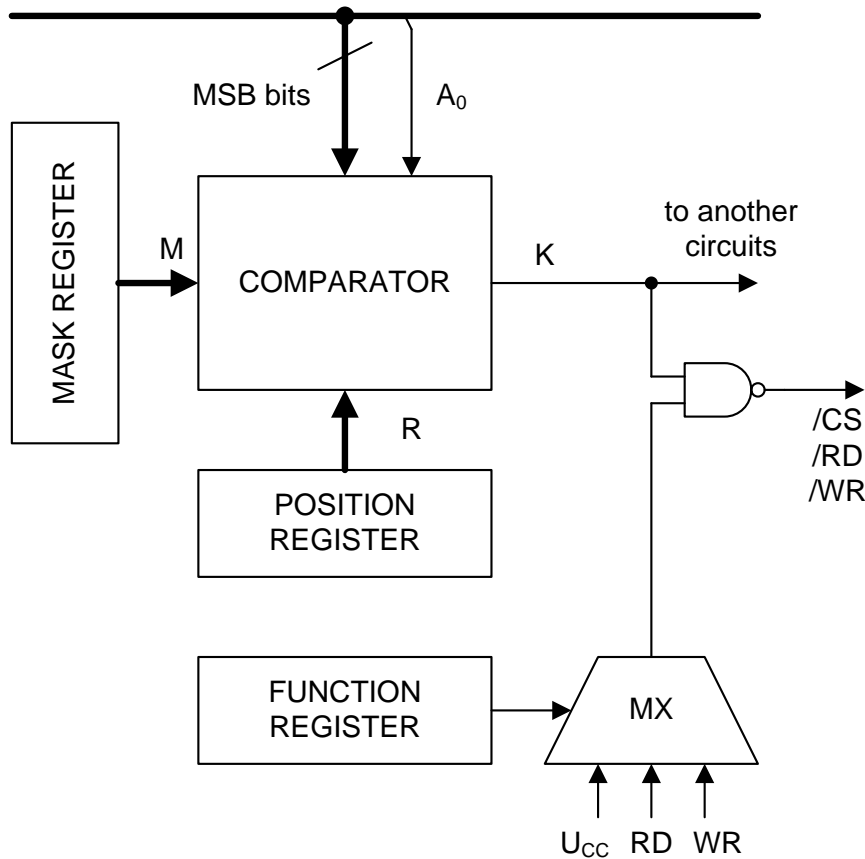

Memory map

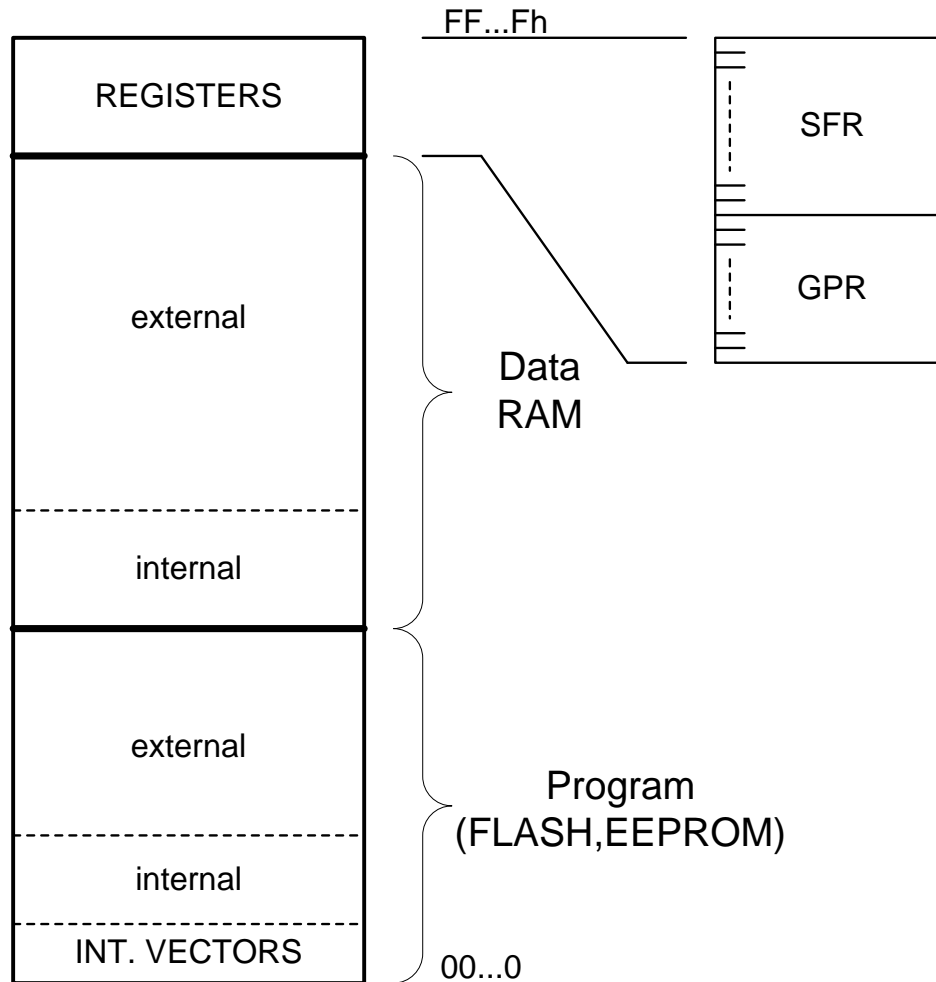

Computer initialization - RESET

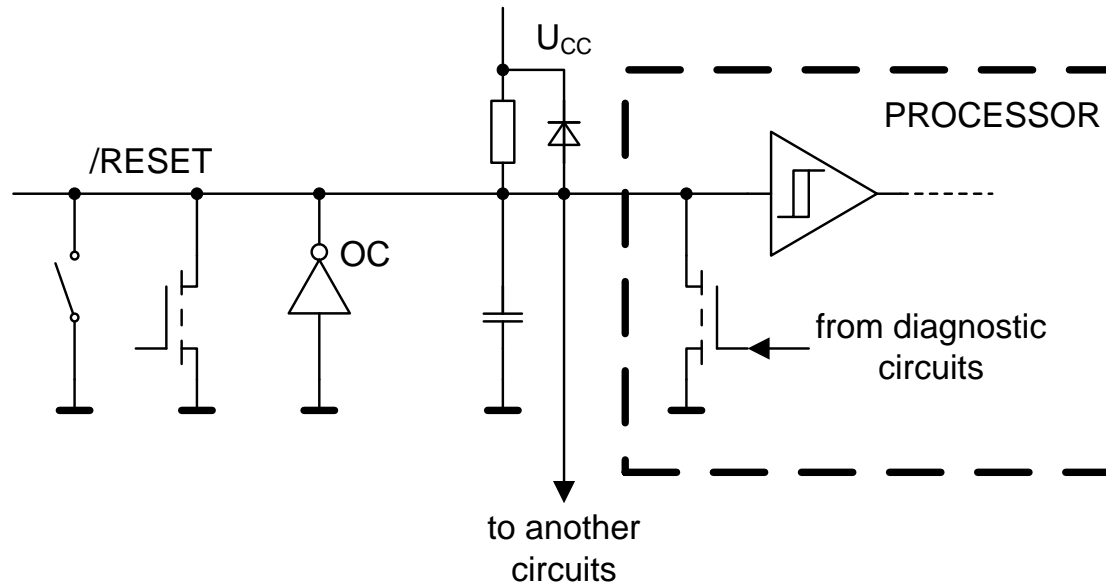

PC = „reset vector“ initial program address


IE = 0 disable interrupts

GPIO set registers to input mode


SP initialization (μP dependent)

GPR, SFR, WDT, BCU (wait, /CSi, addresses) initialization (μP dependent)


μ P clocks

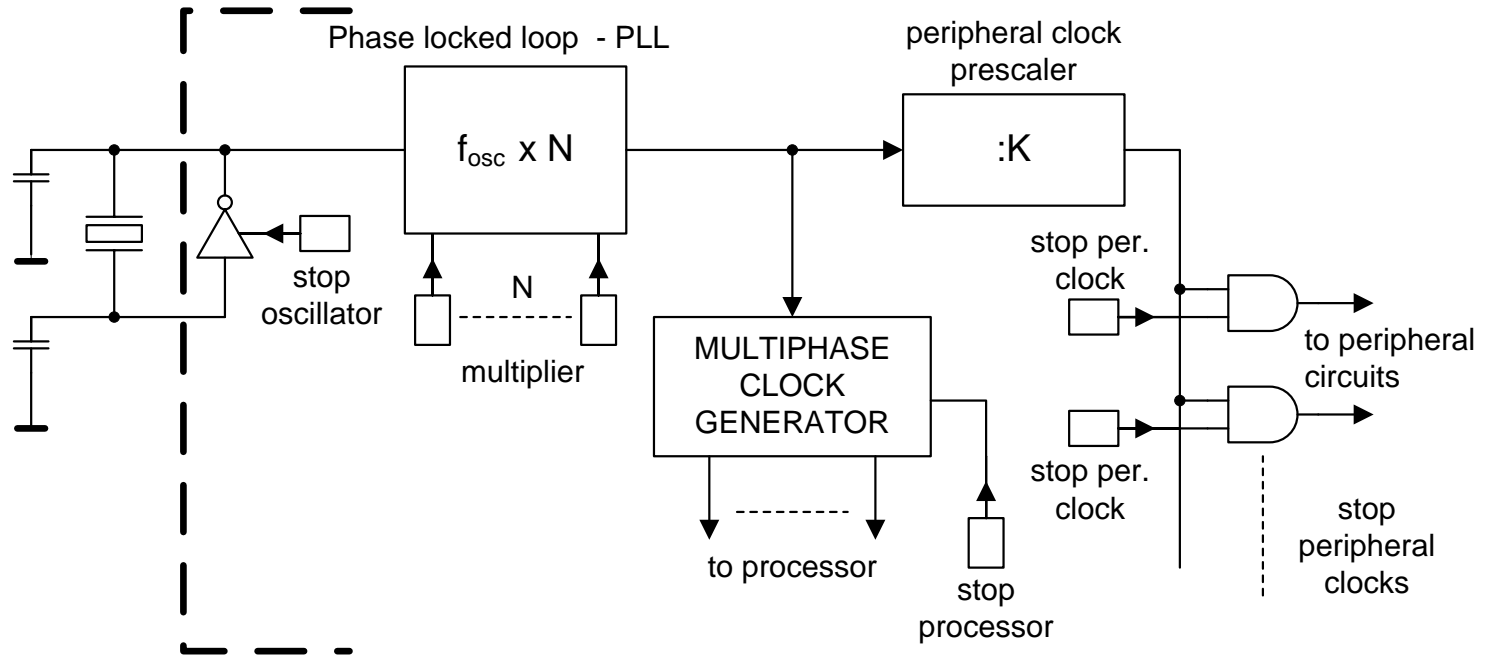

Supervisor – control circuit

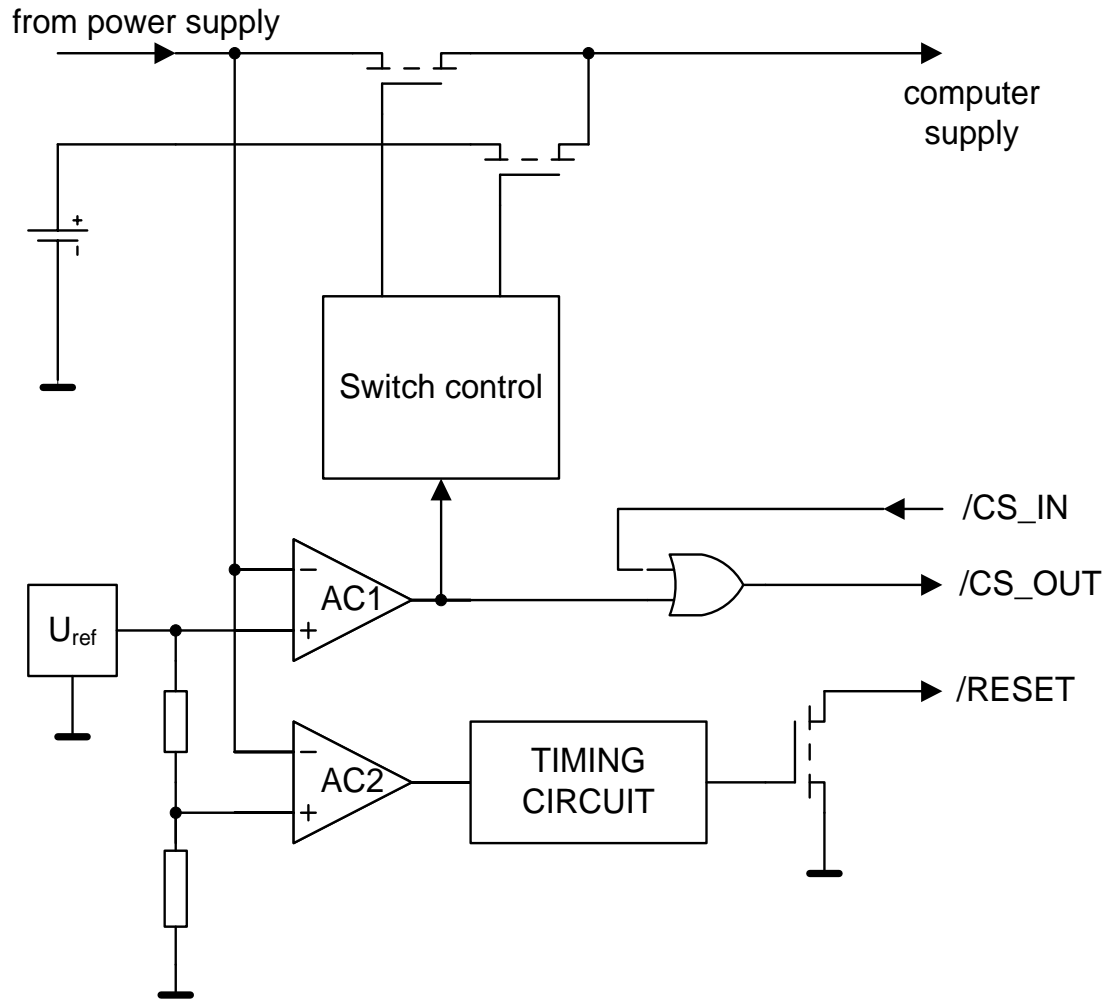

Diagnostic tools of computer

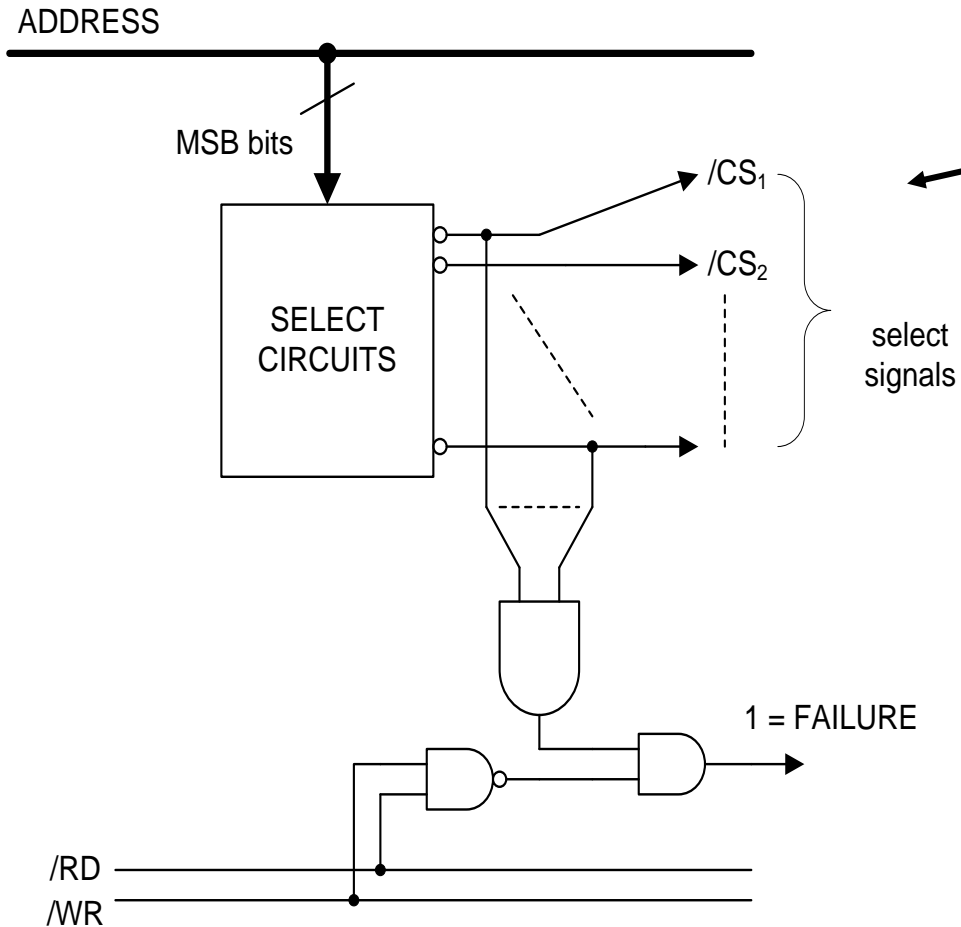

- Valid address check

- Unimplemented instruction codes

- Stack overflow, underflow

Interrupts

Unexpected external event – it can happen any time:

- **asynchronous** signal derived from external processor pin – logical signal
- **asynchronous** request for data processing, coming from external or internal peripheral
- **asynchronous** request coming from processor diagnostic circuits at the exceptions (for example zero division, instruction read error, unimplemented codes...)
- software call – special instruction SWI – debugging and diagnostic purposes


Interrupts

- As a result of unexpected external event processor immediately modifies its activity – stops the main program execution and jumps to the interrupt service routine corresponding the source interrupt vector
- Return address from the Interrupt service routine ISR and important processor's registers are saved onto the stack
- After ISR processing are these ones restored from the stack and program flow returns to the original point

Interrupt types:

- **INT** – mask able – it is possible to disable through global mask
- **NMI** – non mask able – the highest priority

Interrupt controller - external

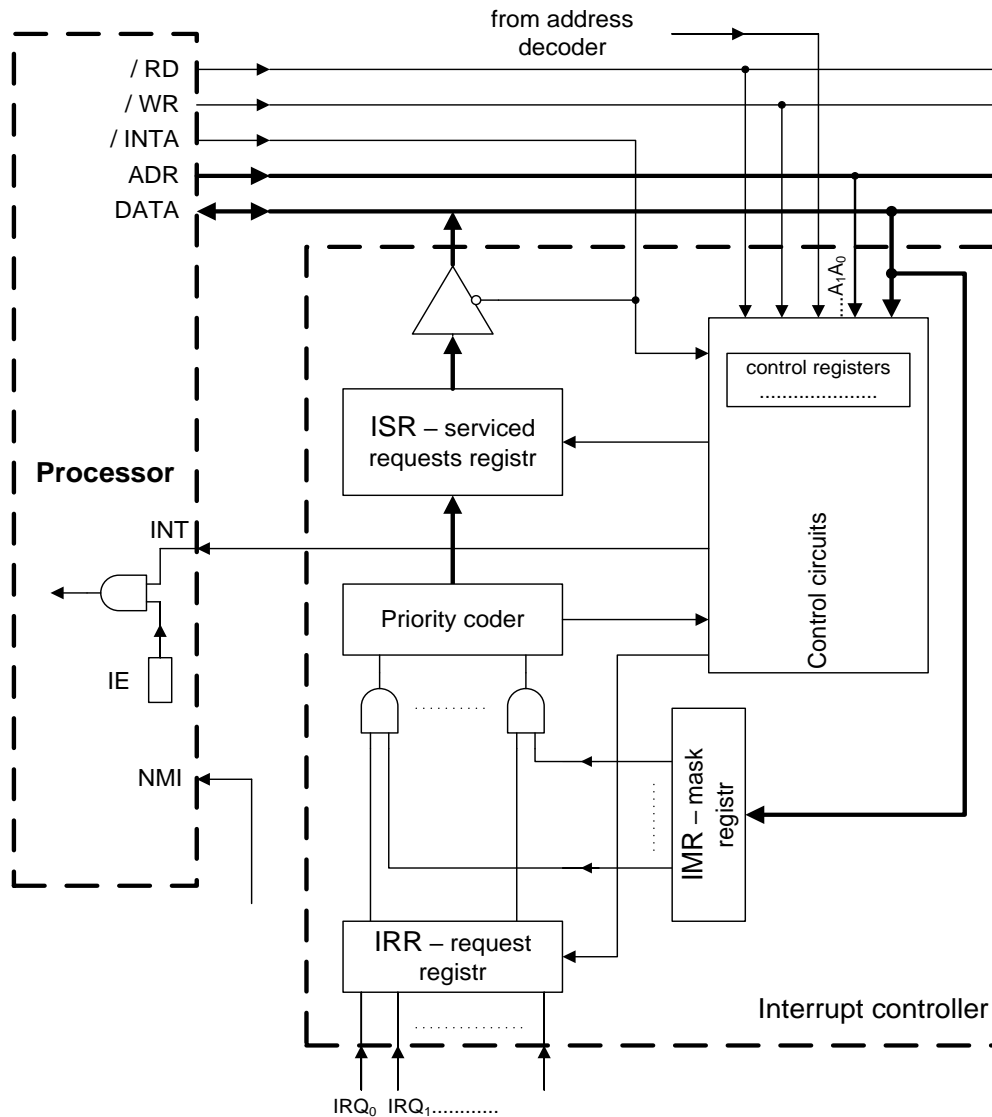

IRR – holds input requests IRQ_i for necessary time prior their processing by the next circuits

IMR – mask interrupt register

ISR – serviced requests registr – it determines interrupt type


IRQ_i – level, edge

IE – interrupt global mask (part of PSW, CCR register)

\overline{INTA} - Interrupt Acknowledge

Interrupt priority

- Fixed
- Cyclic
- Random
- Level based

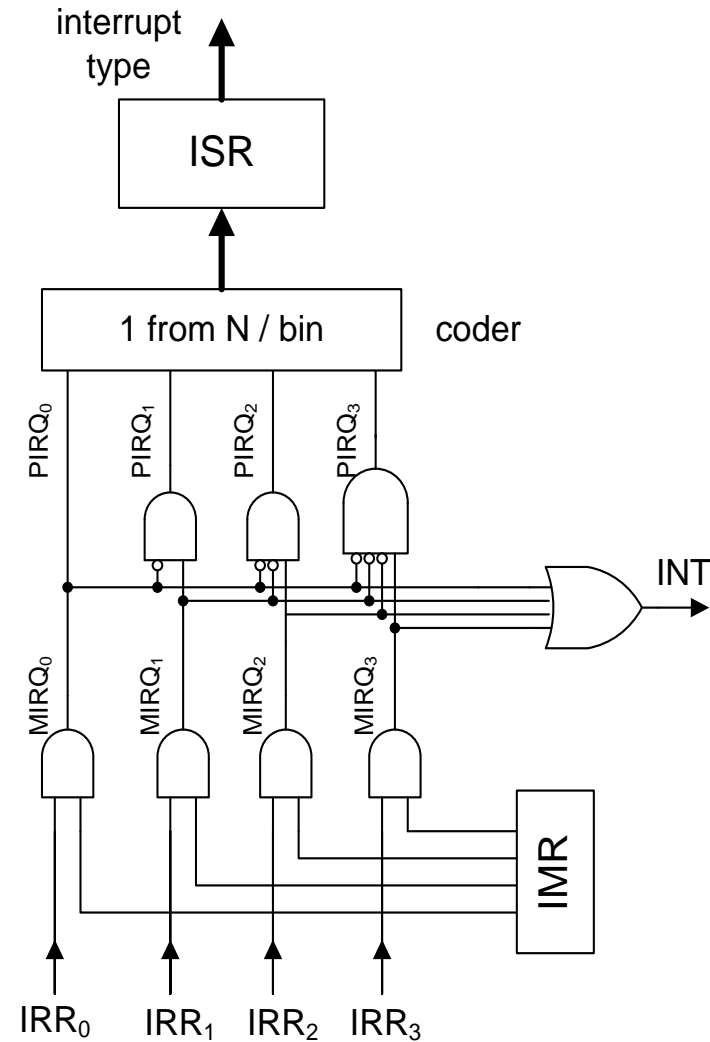


Interrupt level register

level H				IRQ ₃	IRQ ₄		IRQ ₆	IRQ ₇
level L	IRQ ₀	IRQ ₁	IRQ ₂			IRQ ₅		
	← higher priority lower →							

Interrupt sequence

- Provided **IRQi** is not masked and concurrently has got the highest priority, the interrupt request **INT** is generated to processor from interrupt controller
- If global mask **IE** is enabled, interrupt service is started
- Current processing instruction is finished
- The address of instruction following current instruction is saved onto the stack as the return address
- Interrupt type is read by the processor from the interrupt controller's register **ISR** – through signal **INTA**
- Corresponding flip-flop at the register IRR is cleared
- Global interrupt mask **IE** is cleared
- Address assignment - corresponding interrupt service routine address is assigned – ISR vector table, usually in the ROM (FLASH) memory. Control is passed to this routine.
- PSW, accumulator, important registers are saved onto the stack – ISR software is responsible for this activity!!! –**PUSH** instruction
- Global mask **IE** could be optionally enabled for **IRQi** of higher priority processing
- Interrupt service
- All saved registers (PSW, accumulator ...) are restored from the stack – **POP instruction**
- Return to the main program – **RETI** instruction

Single-chip microcomputer interrupts

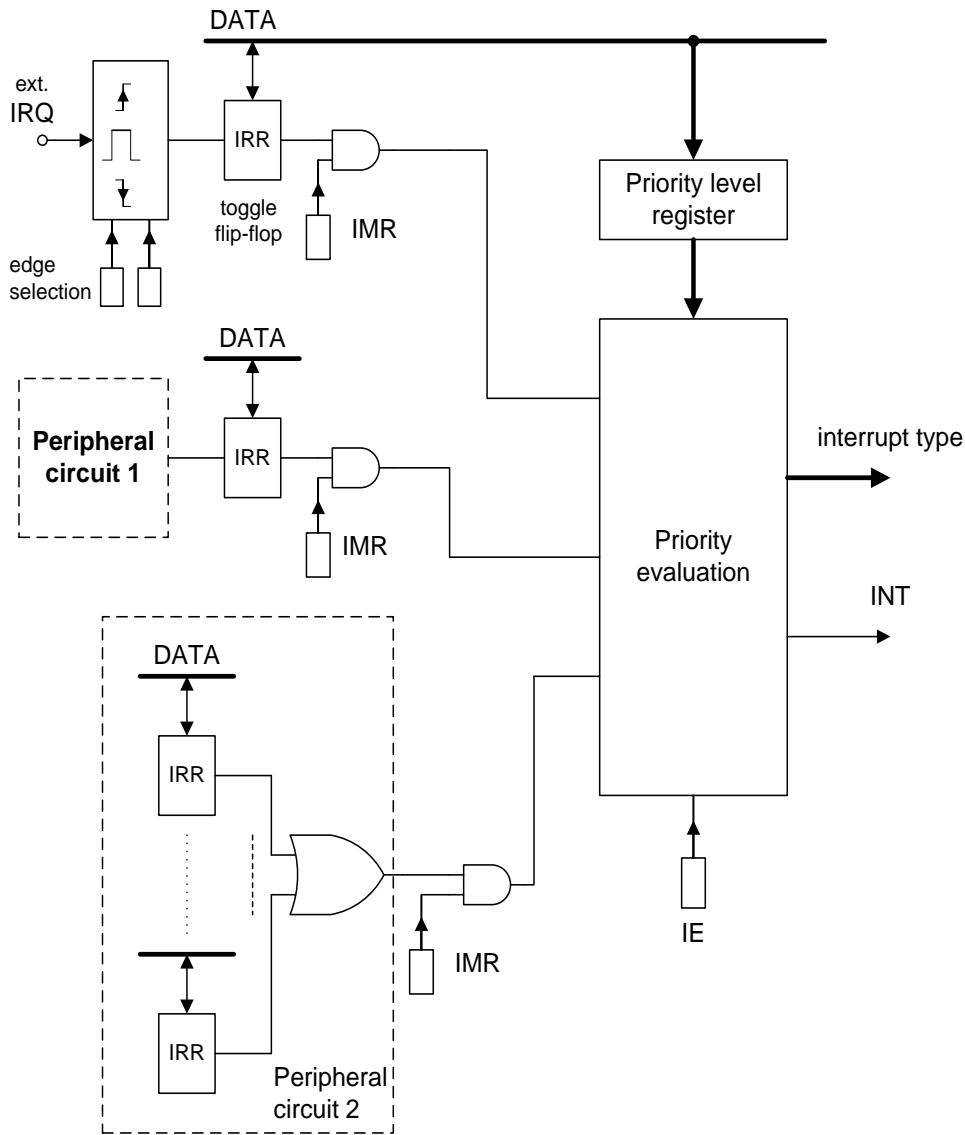


Interrupt circuits connected directly to the peripheral circuits

Processor has got the access to all interrupt controller circuits – not necessary to communicate through the external bus. IRR can be tested by program.

IRR and IMR bits are aggregated either in the common registers or they are included as a part of corresponding control peripheral registers.

Interrupt vectors table

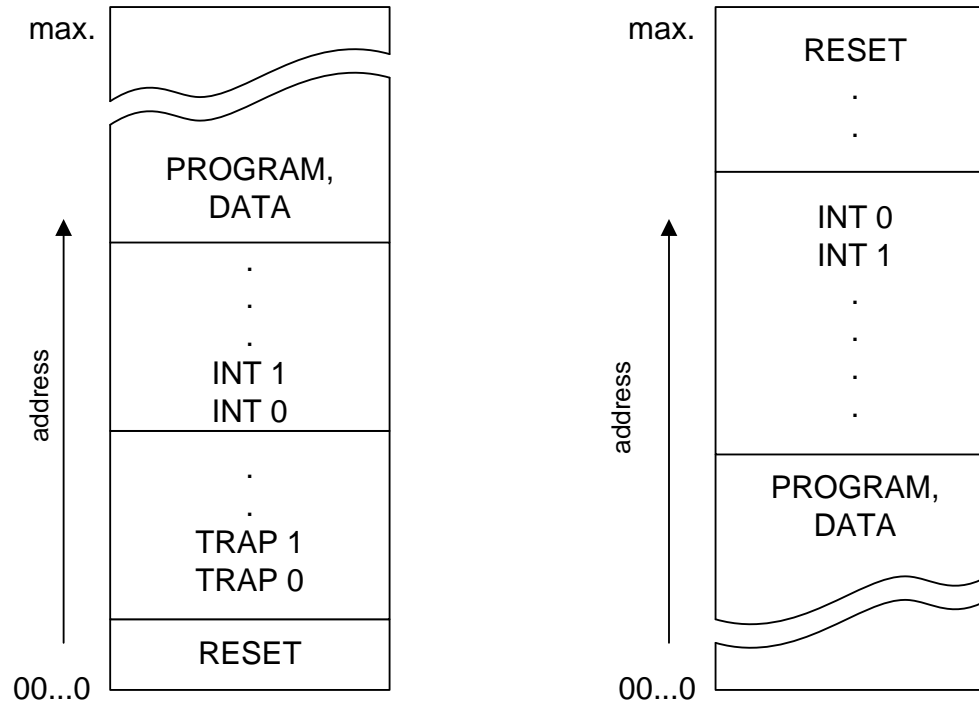

Unused vectors are suitable to service !!!

Interrupt latency

The time from the occurrence of the IRQ request till the time of the first instruction of interrupt service routine execution. Typically several microseconds.

$$Tl_{max} = Tinst_{max} + Tproc$$

Tinst_max – the time of execution of the longest uninterruptable instruction

Tproc - the time for acceptance and processing of the interrupt

Memory

ROM

Mask programmable. The contents is defined during production. Big series

EPROM

Programming - programmer, erasing - UV ultraviolet radiation, reprogramming in order 10^1 x

PROM

EPROM without window – not possible to erase – **OTP** memory

EEPROM

Programming - programmer, in system – per unique addresses. Slow programming (compared to EPROM or FLASH). $10^4 \div 10^5$ x


FLASH

Organized per sectors. Programming - programmer, in system – per unique addresses. Erasing – whole memory or per sector. Higher capacity. $10^4 \div 10^5$ x


RAM

Fast nonvolatile memory. Data and variable storage. Static – CMOS, dynamic - PC

External memory

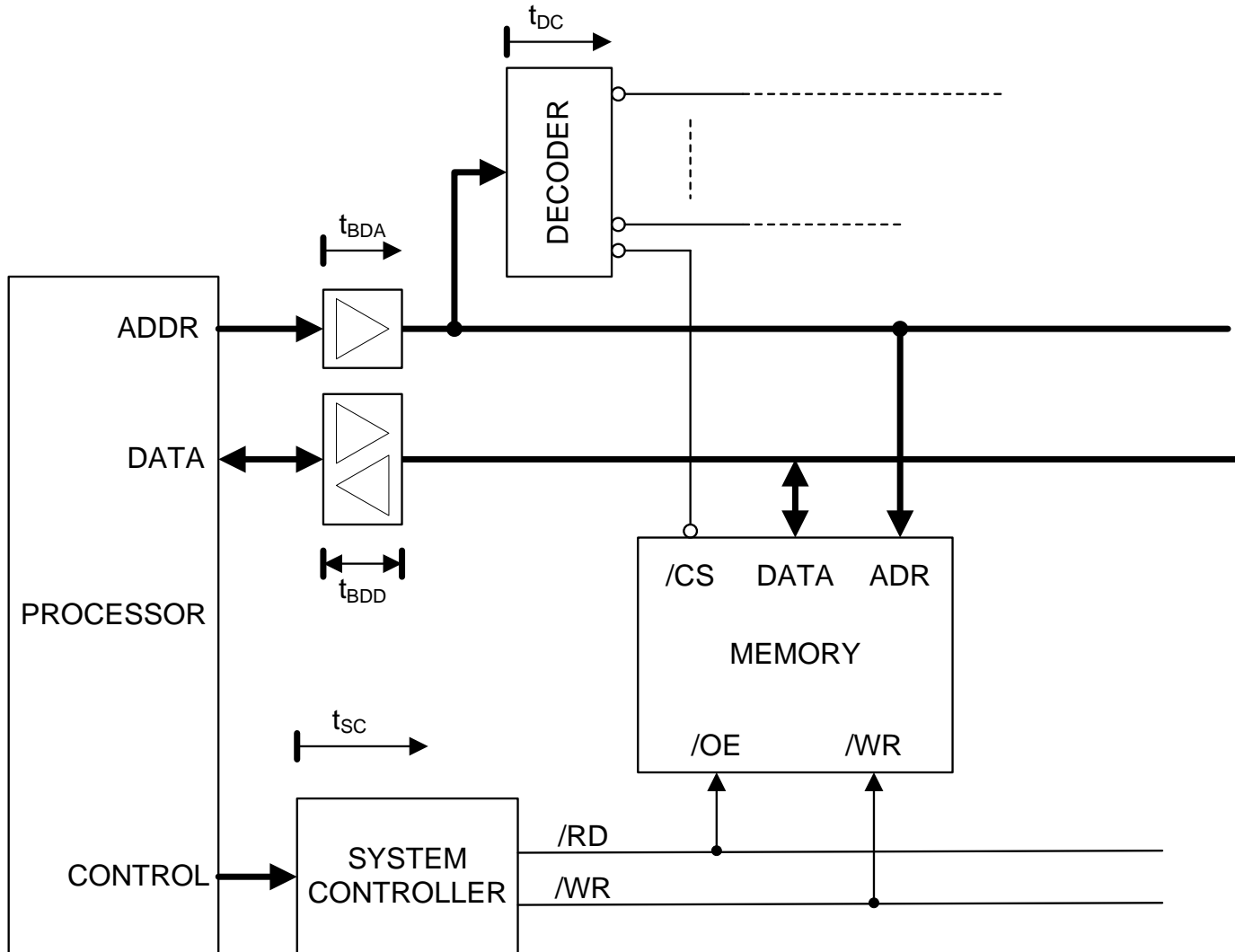


Memory overlapping

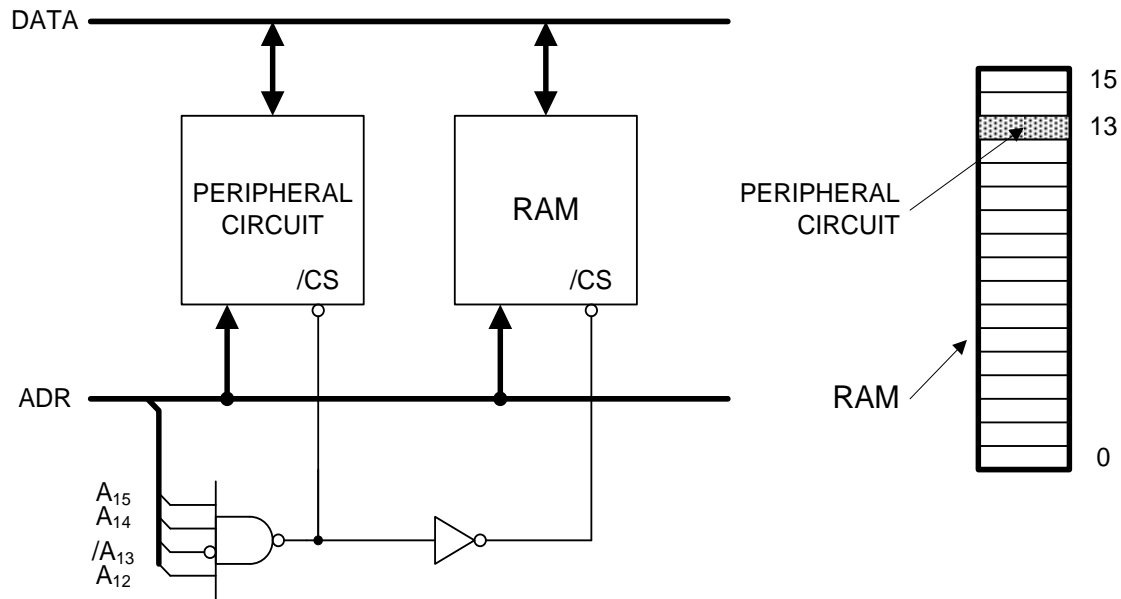


1101 XXXX XXXX XXXX_B

Peripheral address space


Controlled overlapping – shadow ROM

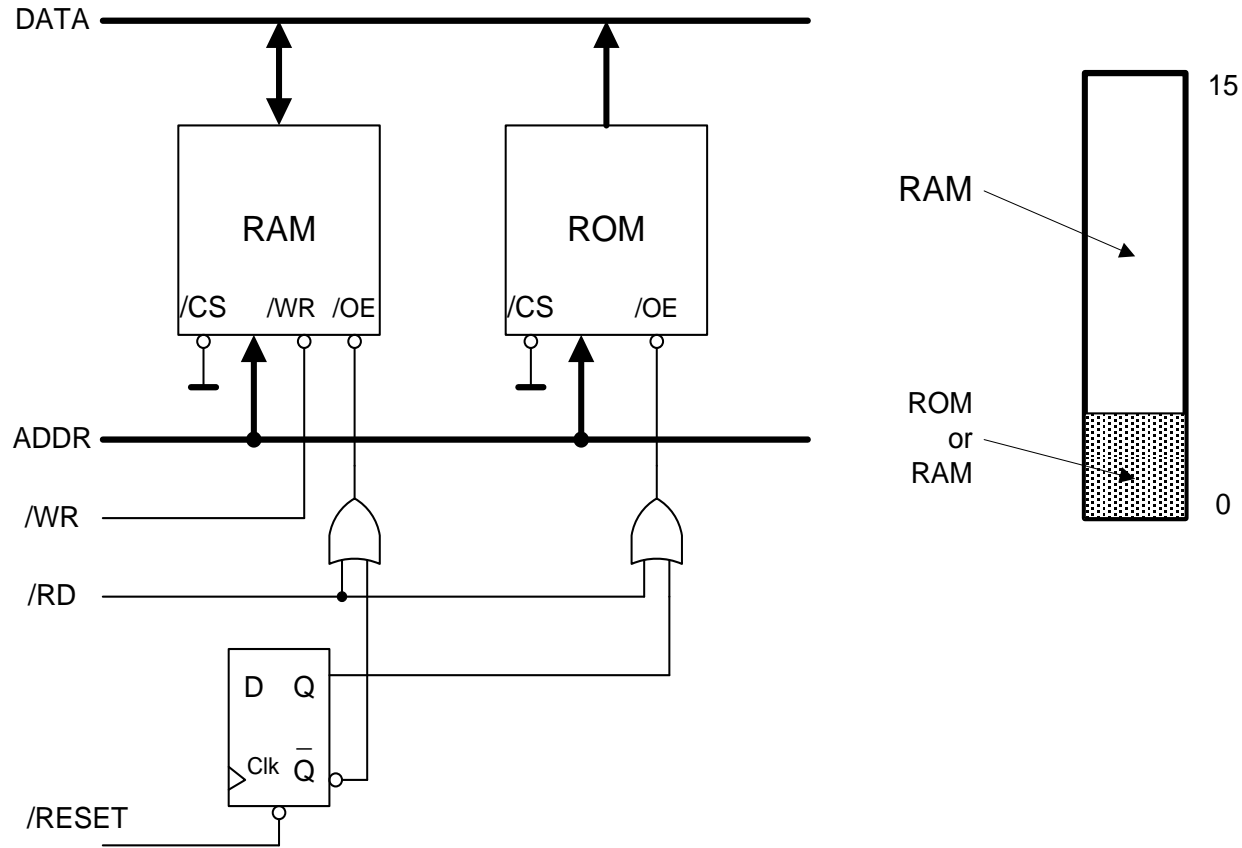

In system FLASH memory programming

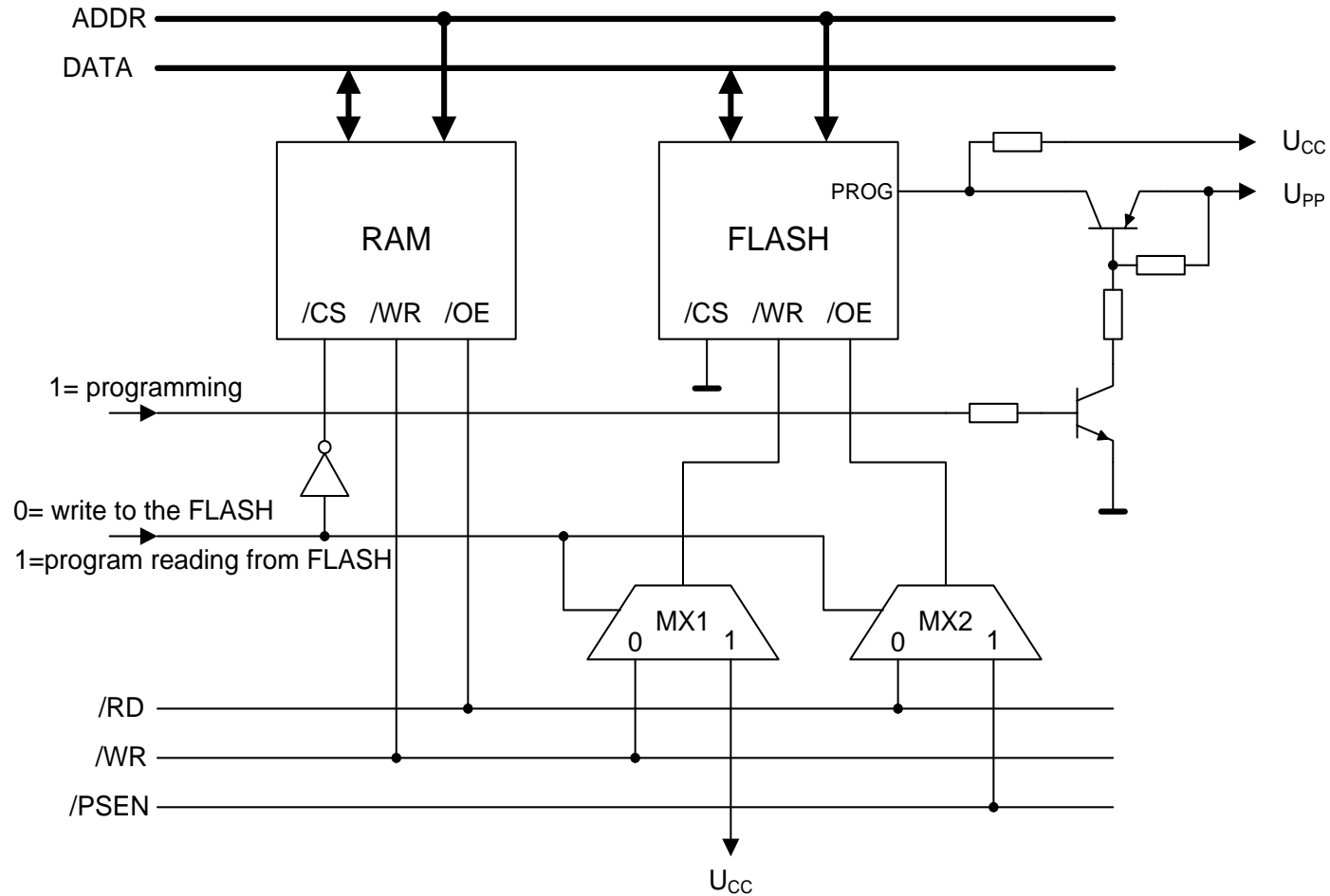


Direct memory access - DMA

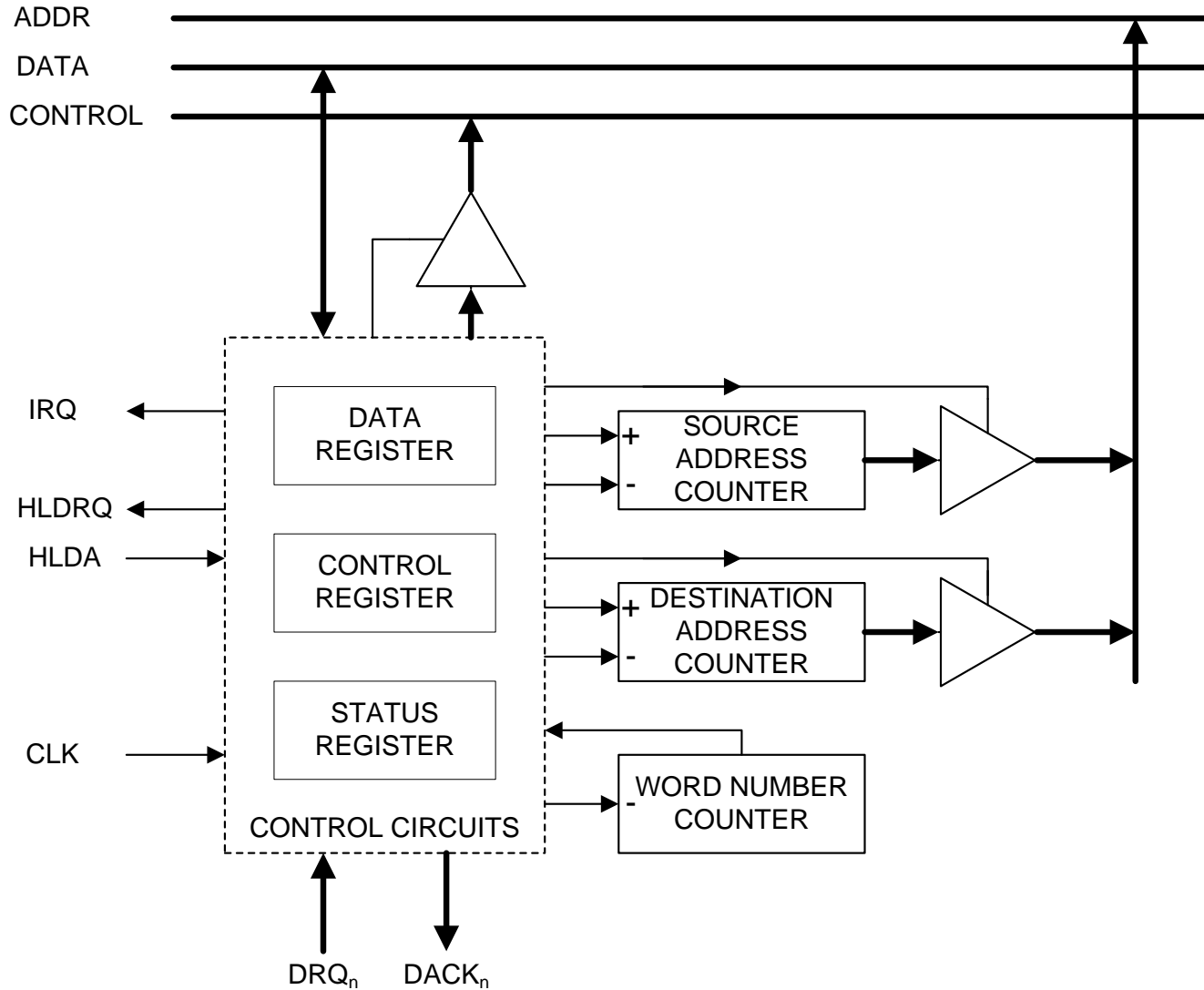


Timers - counters

- Important and necessary for real-time control applications
- Time functions generation, precision timing signals, external events counting, program synchronization on external events ...
- **Multi-chip solution** – HW configuration flexibility
- **Single-chip microcomputer** – internal structure configurable through SFRs
- Usually 16-bit
- More timers-counters aggregated into the one configurable system
- Connection to the internal interrupt system of microprocessor

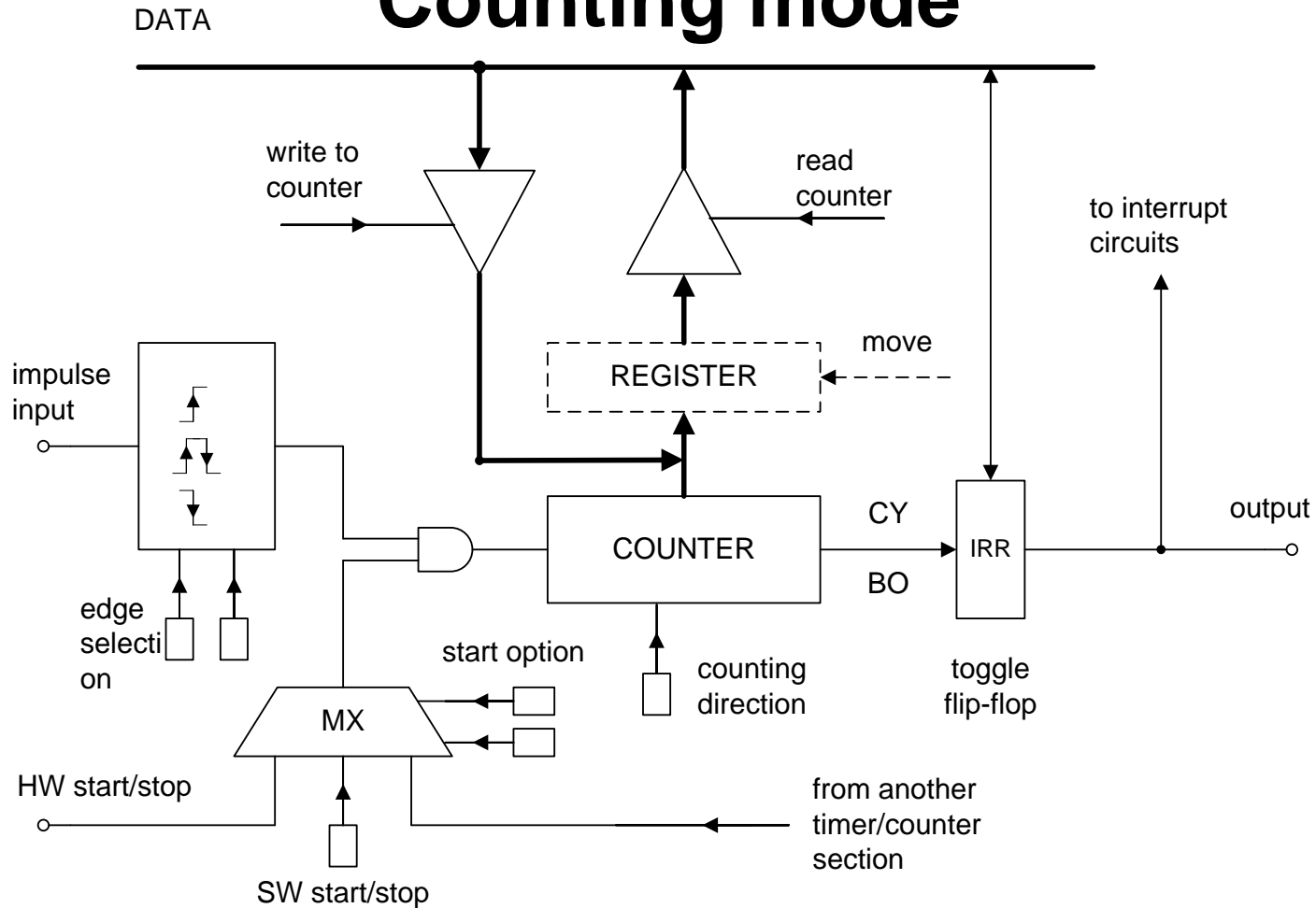Generally purposed timer-counter (GPT) Counting mode




Synchronous edge detector

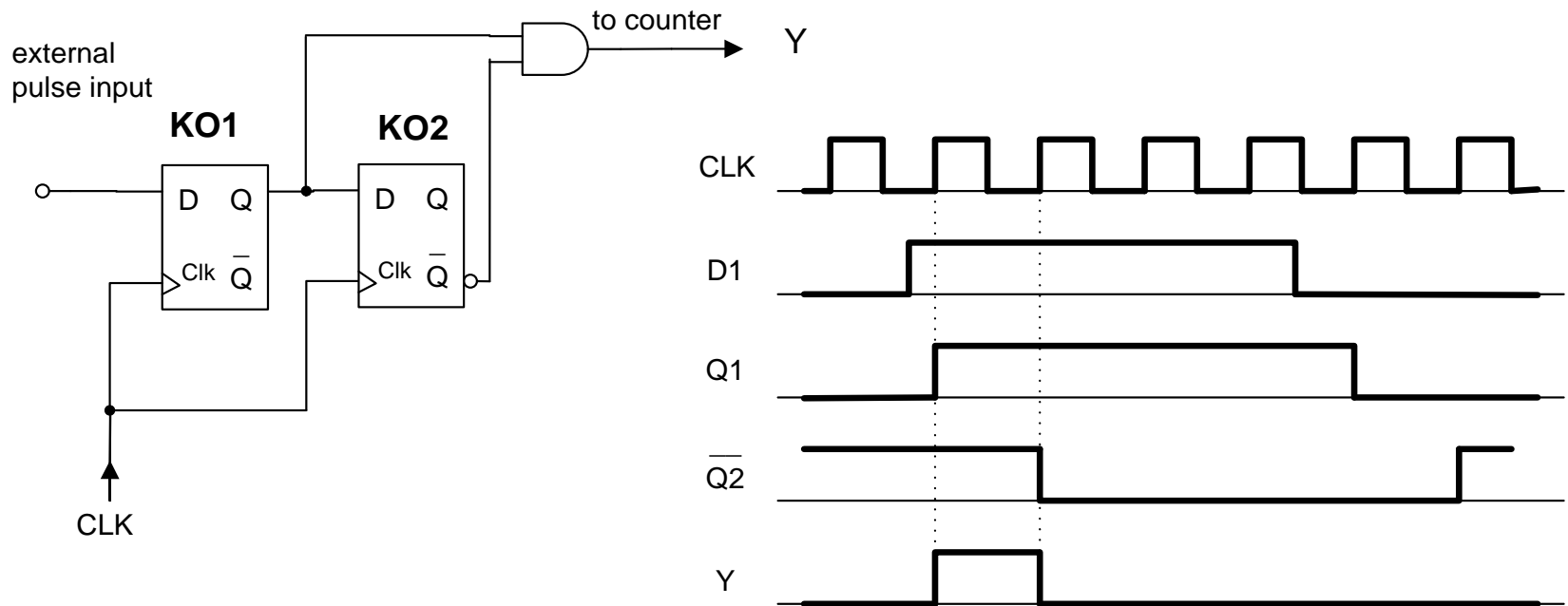


Generally purposed timer-counter (GPT)


Timing mode

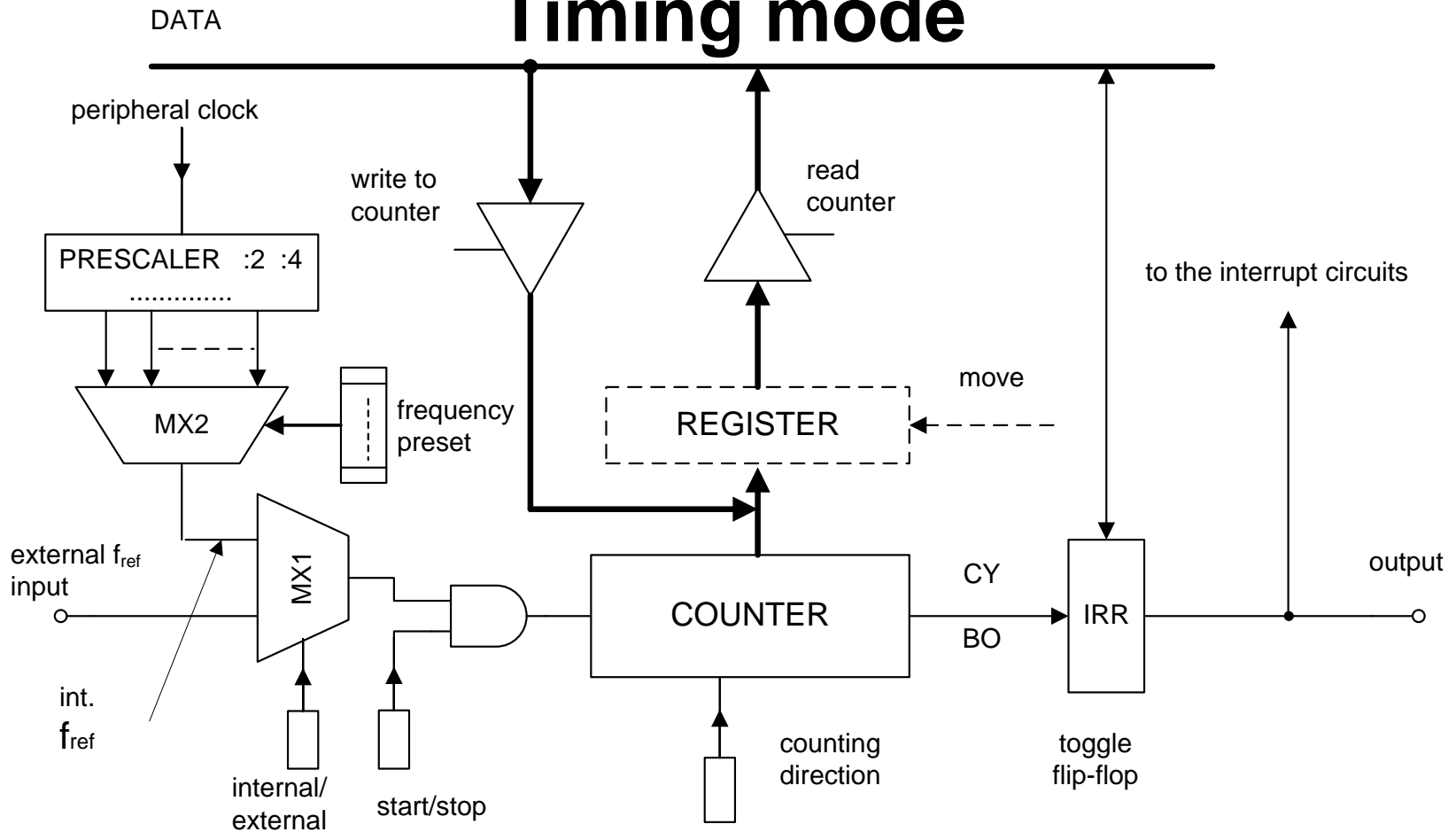



Capture – Compare Unit

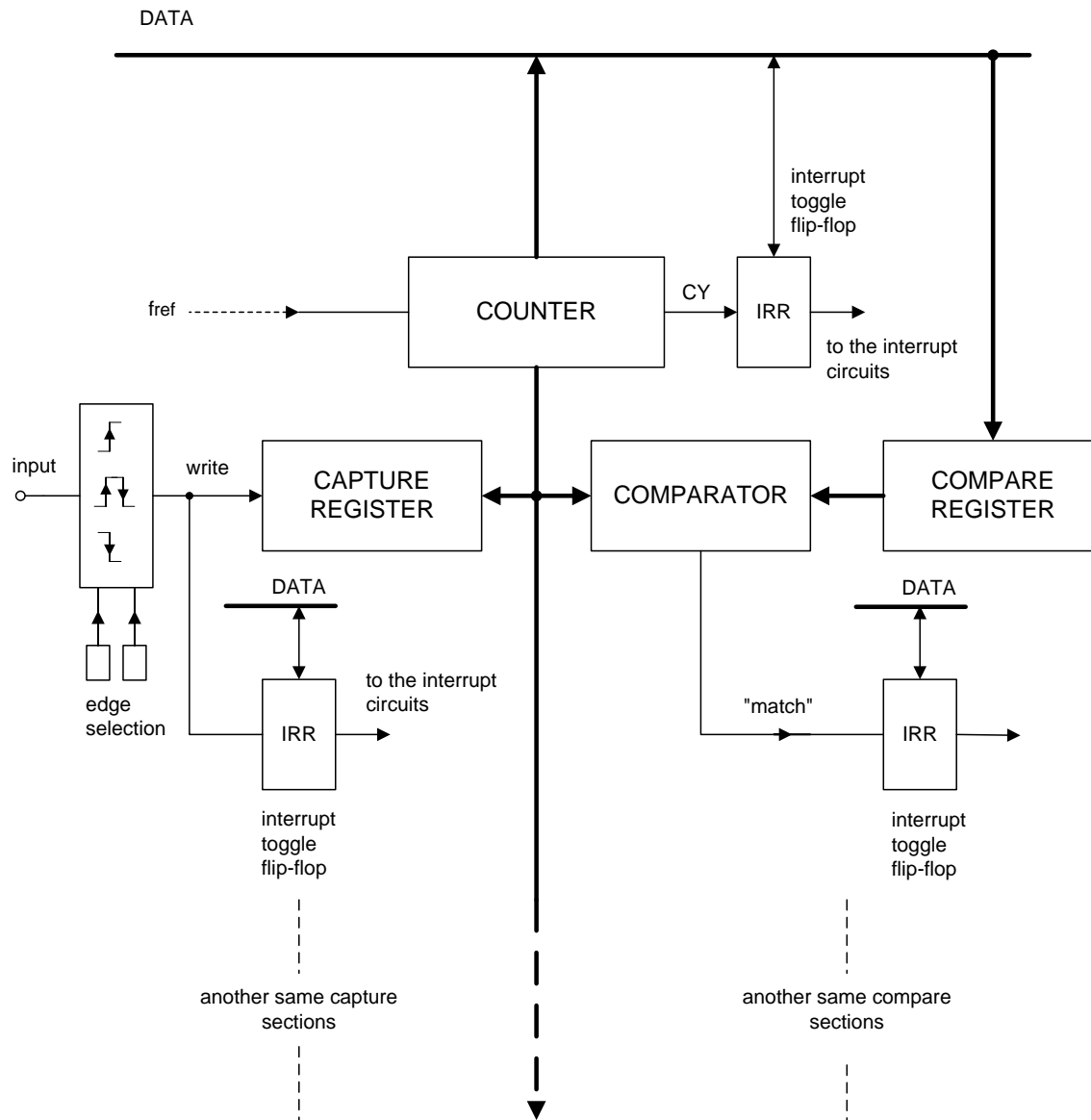


PWM modulation

 

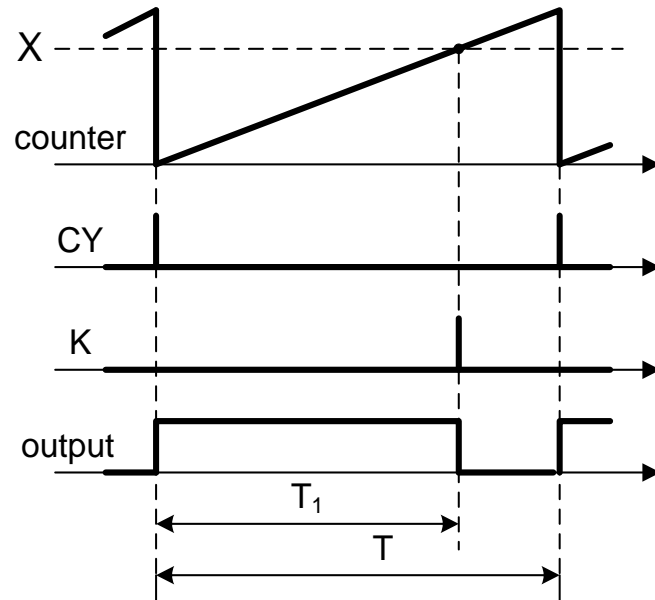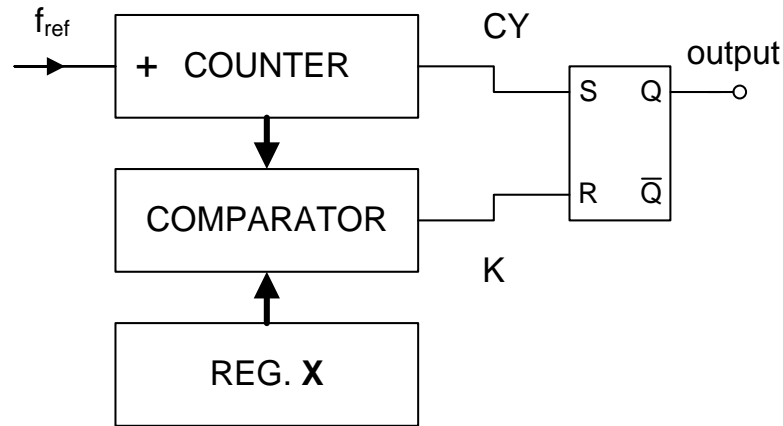
$$U_{STR} = \frac{T_1}{T} (U_H - U_L) + U_L$$




PWM demodulation

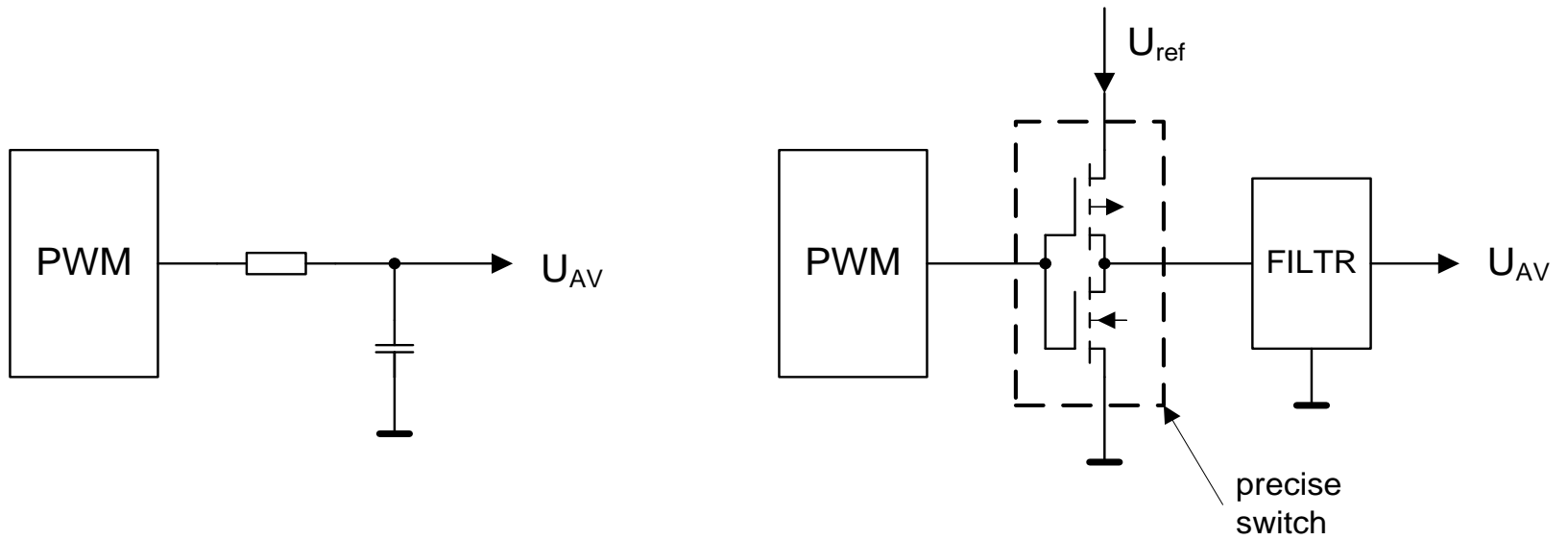



Parallel input circuit

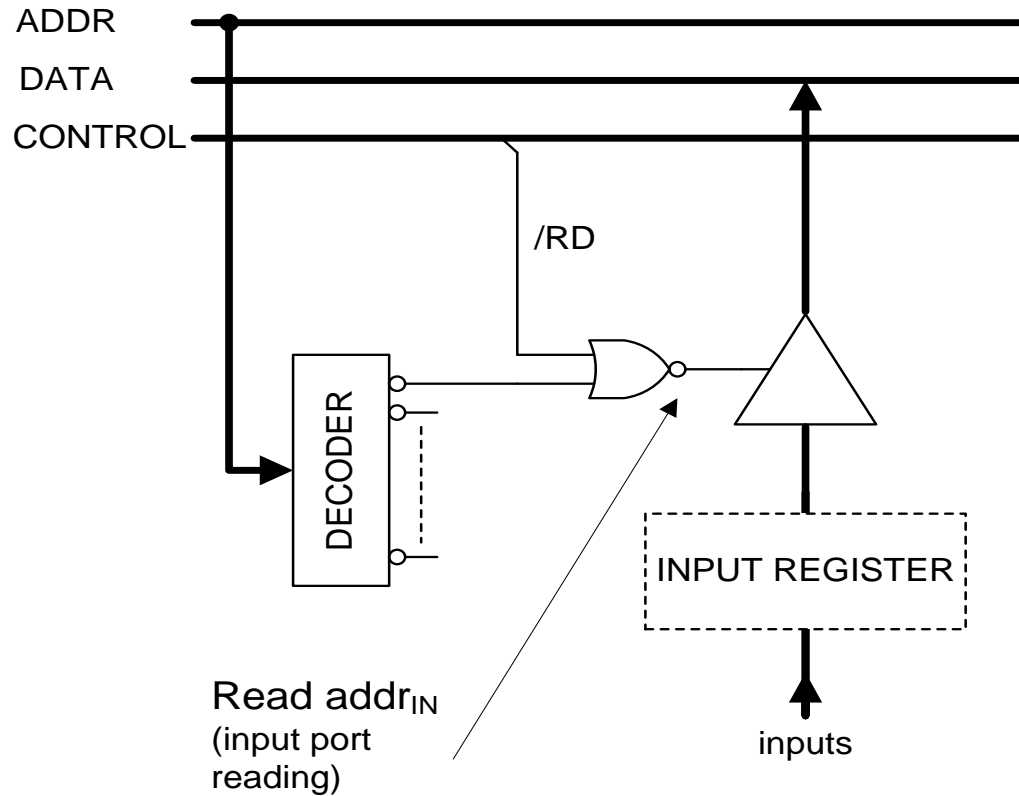


Parallel output circuit

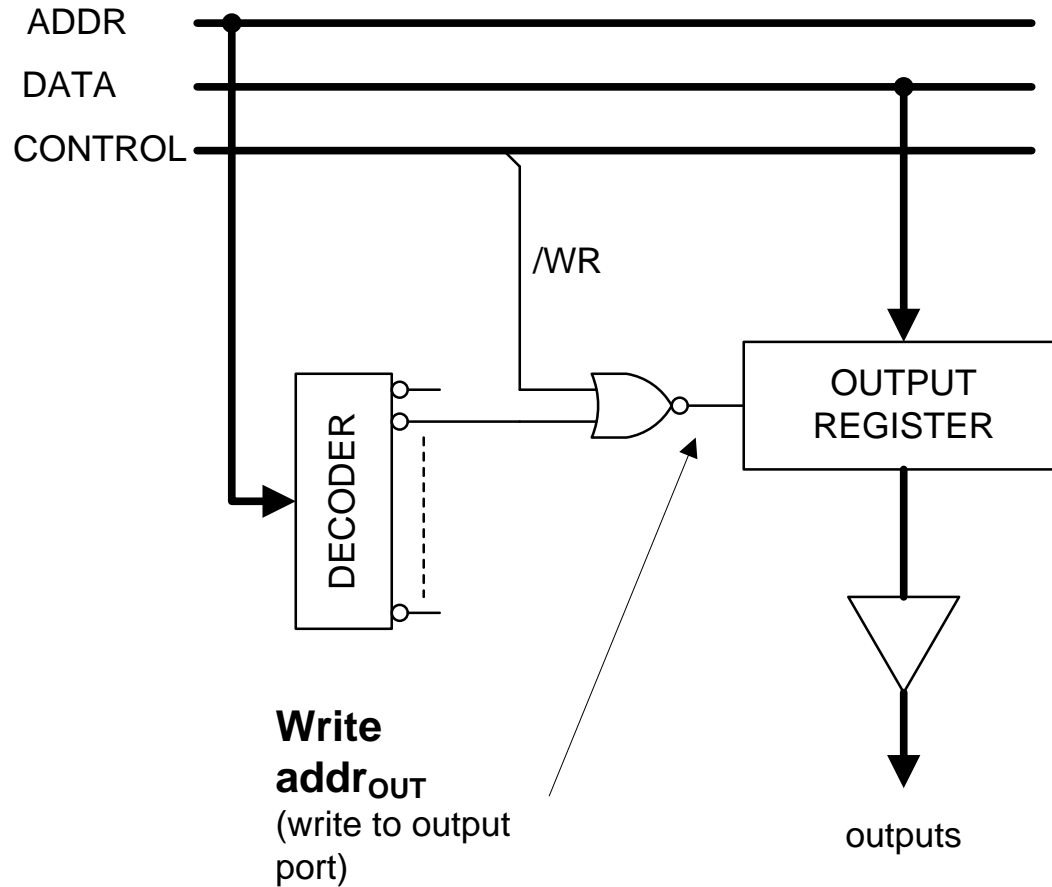





Handshake

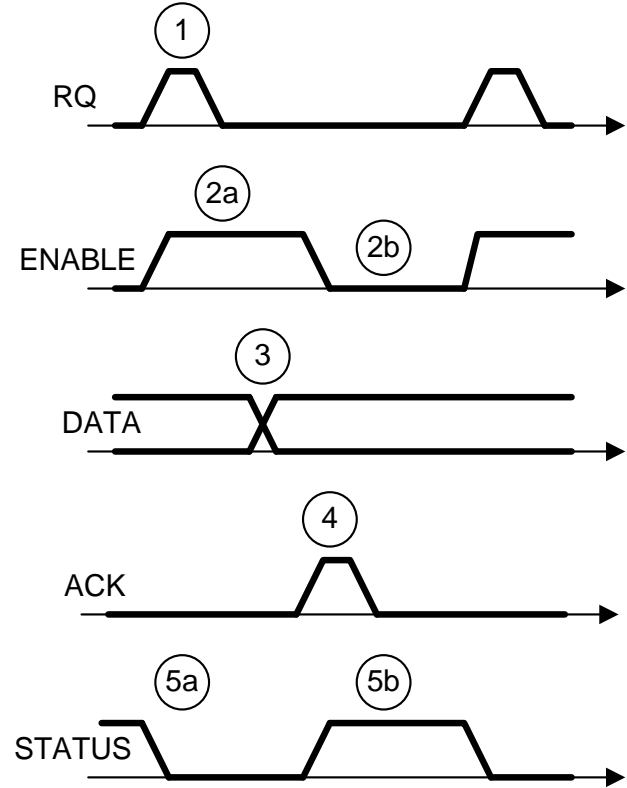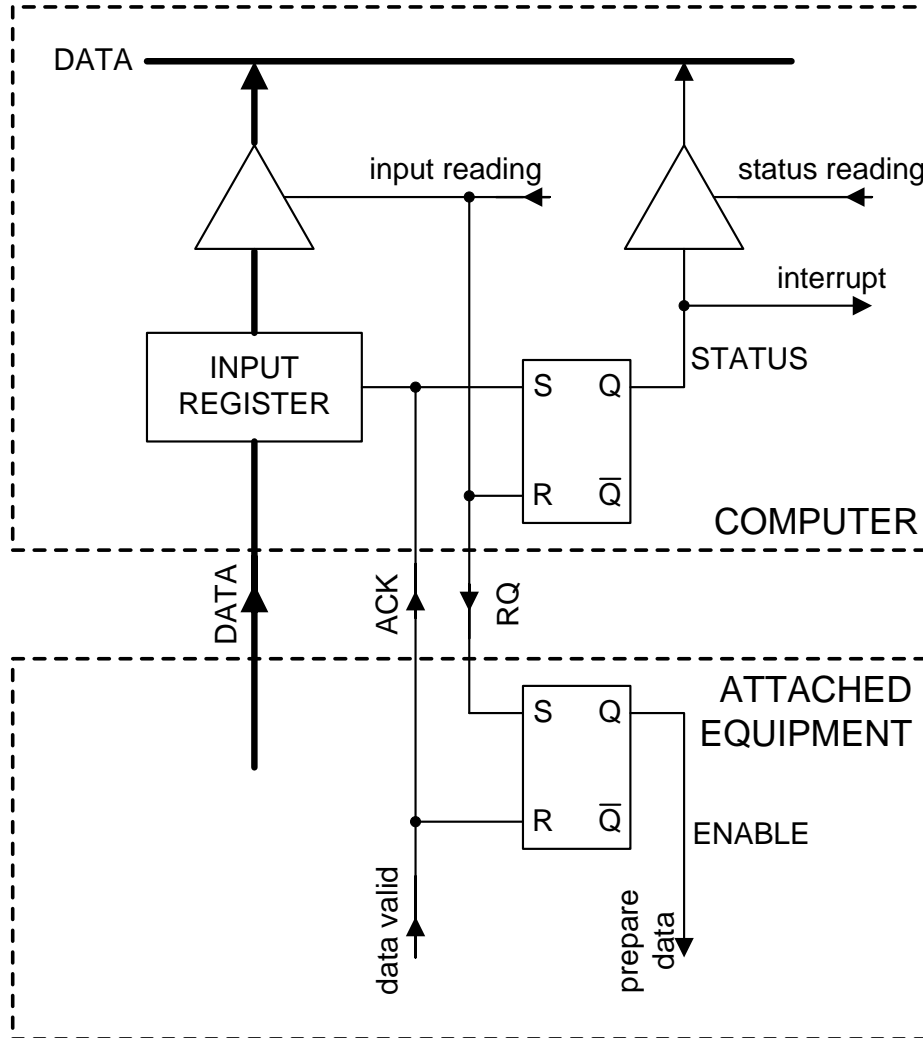


Bidirectional I/O port – 1 bit

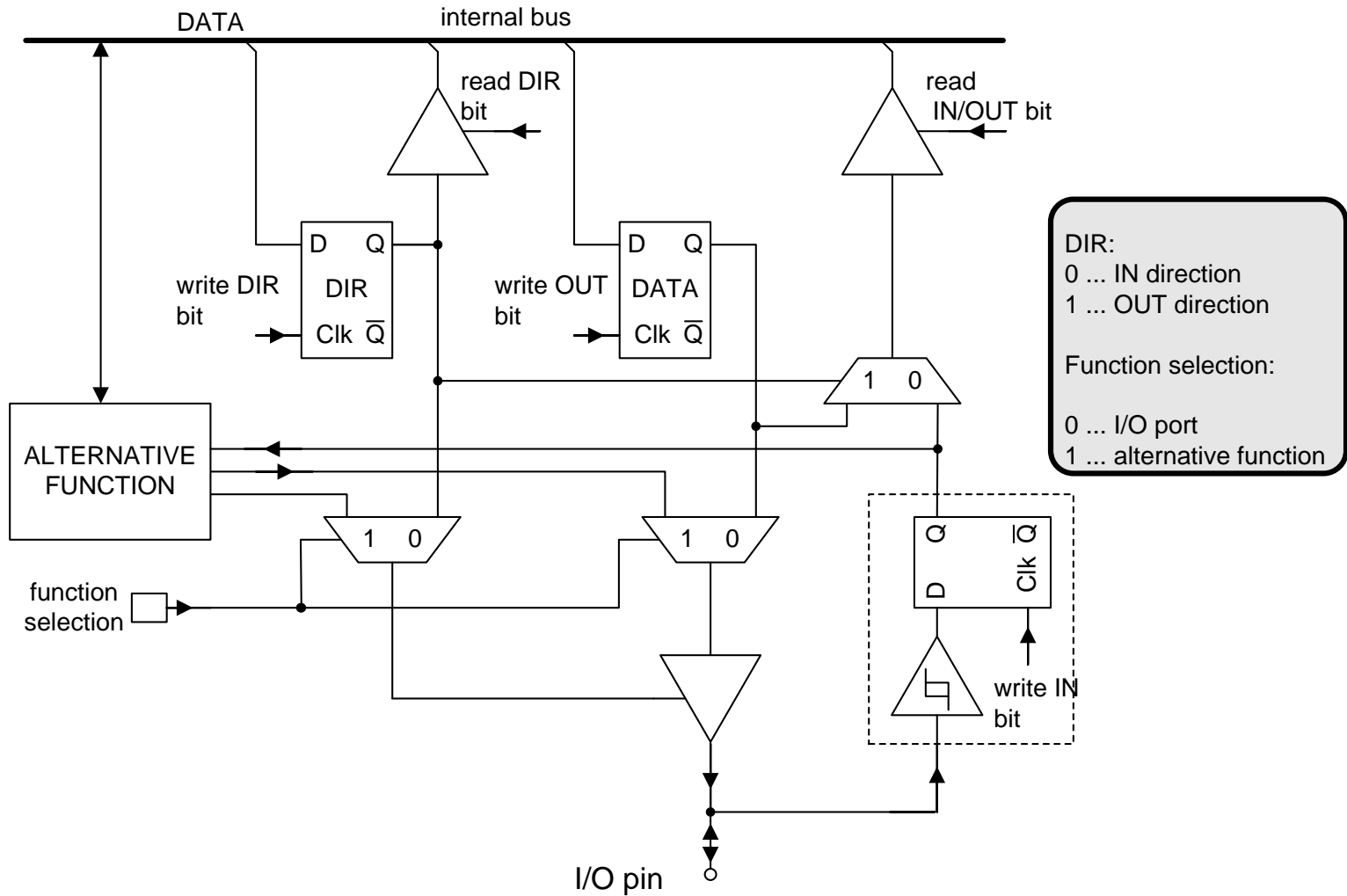




Output port circuit

   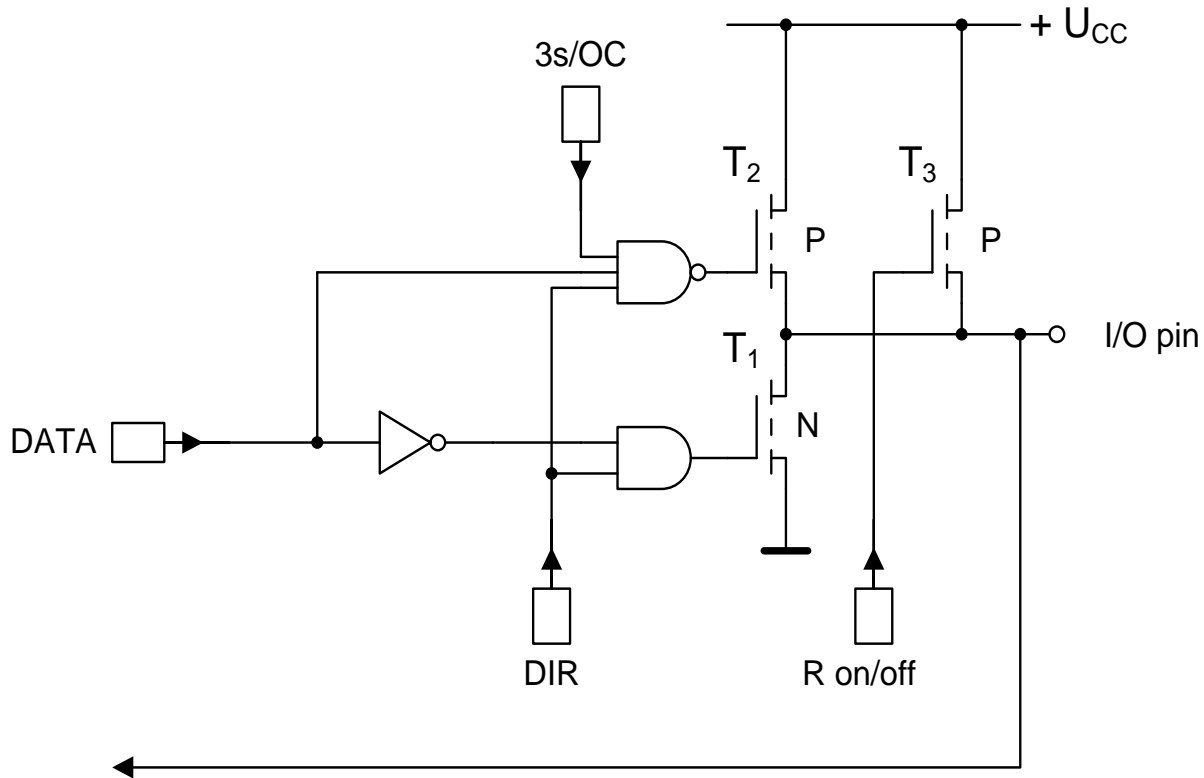


Serial communication

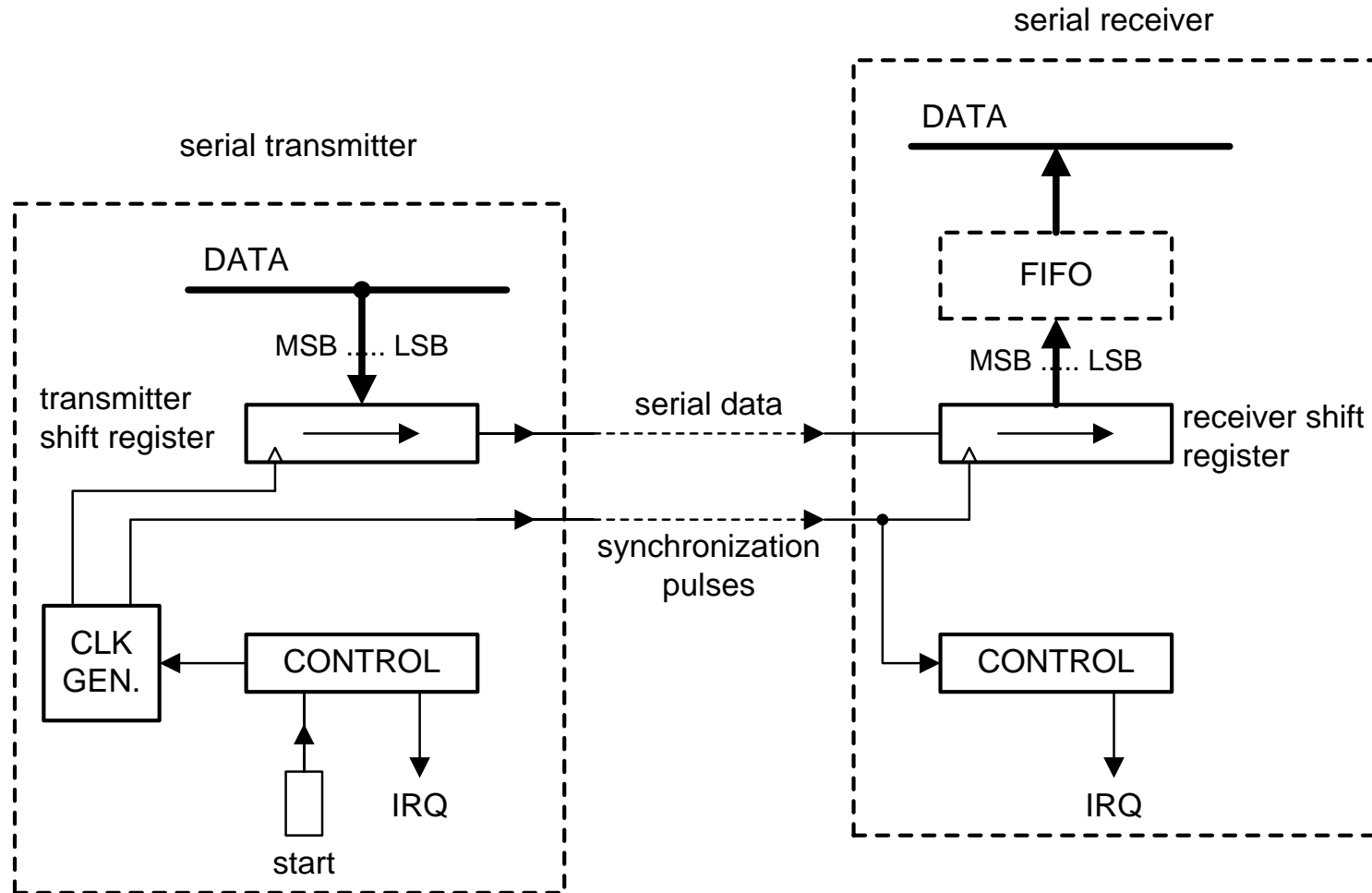

Serial data sampling

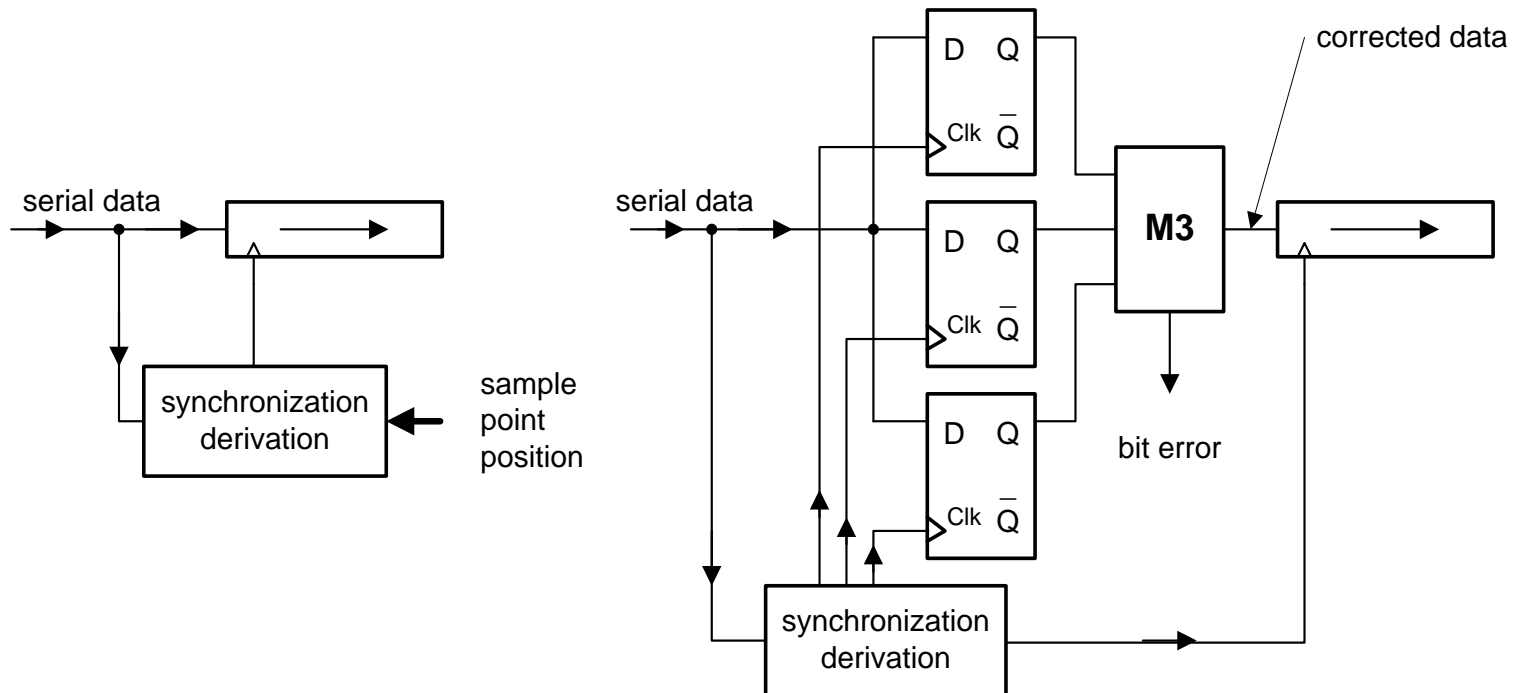  


Character synchronization

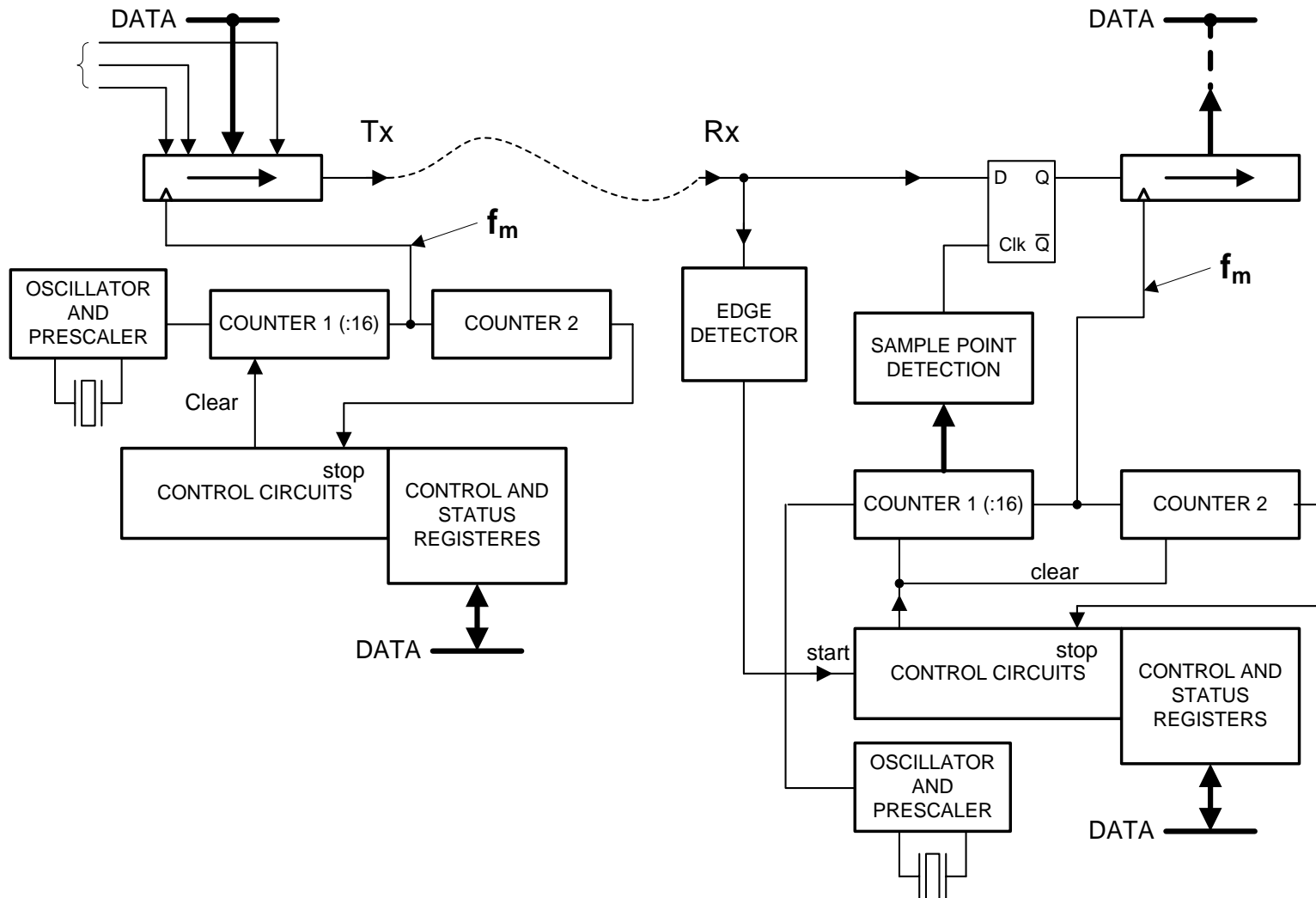

UART

 Universal Asynchronous Receiver - Transmitter



Number of data bits optional (typically 7 - 9) – LSB first

Parity bit – peripheral dependent

Number of stop bits optional (1 - 2)


Error detection - bit error samples mismatch

- parity error

- frame error stop bit equals 0

- dat lost overrun error

RS232

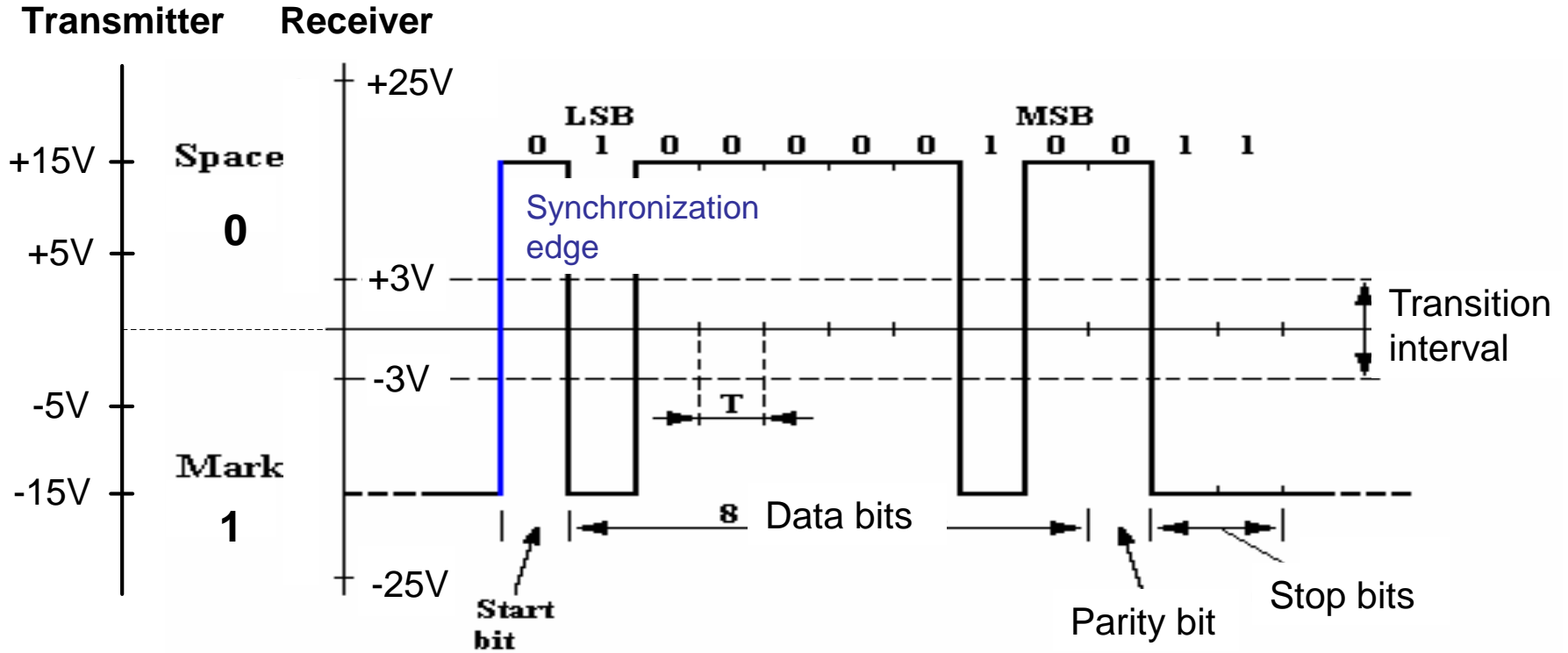

RS232 - features

- point to point duplex asynchronous communication
- asymmetric line
- negative logic
- input and output impedance of the transmitter and receiver in the range $3 \div 7 \text{ k}\Omega \gg$ terminating line impedance
- Slew rate of the signal $30\text{V}/\mu\text{s}$ at maximum
- Baud rate determined by maximal load capacitance of the line 2500 pF ($166,7 \text{ pF/m}$):
 - 19,2 kbit/s at 15 m length
 - 115,2 kbit/s at 3 m length

Thank for your attention...